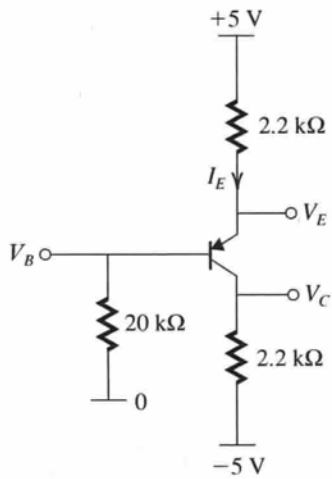


6.60



If active, $|V_{BE}| = 0.7 \text{ V}$

$$I_B = \frac{5 - 0.7}{20 \text{ k}\Omega + (\beta + 1)2.2 \text{ k}\Omega} = 0.0325 \text{ mA}$$

$$V_B = 20 \text{ k} \times 0.0325 = 0.65 \text{ V}$$

$$V_E = V_B + 0.7 \text{ V} = 1.35 \text{ V}$$

$$V_C = -5 + \beta I_B 2.2 = -1.425 \text{ V}$$

$$|V_C - V_E| = 2.78 \text{ V} > 0.4$$

\therefore active mode


Largest R_C for active mode

$$V_C = V_E - 0.3 \text{ V} = 1.35 - 0.3 = 1.05 \text{ V}$$

$$I_{C\text{max}} = \frac{1.05 - (-5)}{2.2 \text{ k}} = 2.75 \text{ mA}$$

6.63

(a)

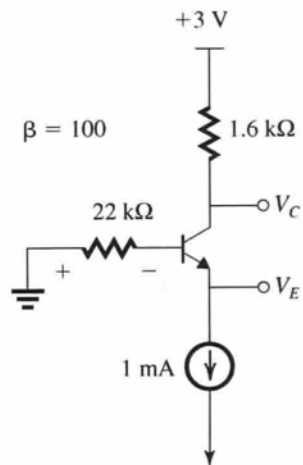

$$I_B = I_E / (\beta + 1) = 0.0099 \text{ mA}$$


$$V_B = 0 - I_B \times 22 \text{ k} = -0.22 \text{ V}$$

$$V_E = V_B - 0.7 = -0.92 \text{ V}$$

$$I_C = \beta I_E / (\beta + 1) = 0.99 \text{ mA}$$

$$V_C = 3 - 0.99 \times 1.6 = 1.42 \text{ V}$$

(b)

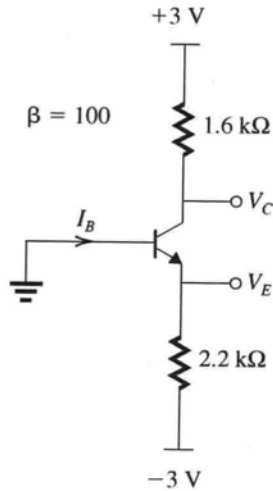

$$V_B = 0$$


$$V_E = V_B - 0.7 \text{ V} = 0.7 \text{ V}$$

$$I_E = \frac{-0.7 - (-3)}{2.2} = 1.05 \text{ mA}$$

$$I_C = \beta I_E / (\beta + 1) = 1.04 \text{ mA}$$

$$V_C = 3 - 1.04 \times 1.6 = +1.34 \text{ V}$$

(c)

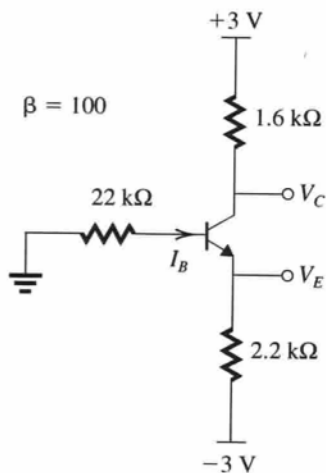

$$\beta = 100$$

$$I_E = \frac{0 - 0.7 - (-3)}{2.2 + 22/101} = 0.95 \text{ mA}$$


$$V_E = -3 + 0.95 \times 2.2 = -0.91 \text{ V}$$

$$V_B = V_E + 0.7 = -0.21 \text{ V}$$

$$[V_B = 0 - 22 \times 0.95 / 101]$$

$$V_C = 3 - 1.6 \times 0.95 \times \frac{100}{101} = +1.5 \text{ V}$$

(d)

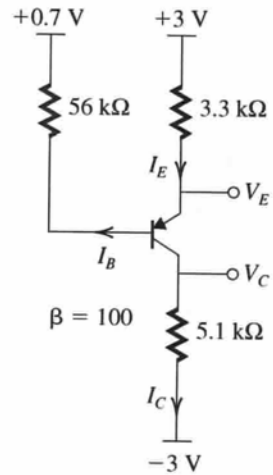


$$I_E = \frac{3 - 0.7 - 0.7}{3.3 + 56/101} = 0.42 \text{ mA}$$

$$V_E = 3 - 0.42 \times 3.3 = +1.6 \text{ V}$$

$$V_B = V_E - 0.7 \text{ V} = +0.9 \text{ V}$$

$$V_C = -3 + 5.1 \times 0.42 \times \frac{100}{101} = -0.88 \text{ V}$$

(e)

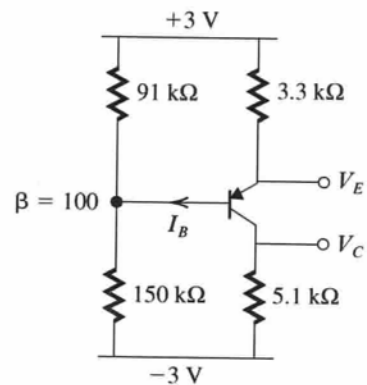

Let

$$V_{BB} = -3 + \frac{150 \times 6}{150 + 91} = +0.73 \text{ V}$$

$$R_{BB} = 91 \parallel 150 = 56.6 \text{ k}\Omega$$

$$I_E = \frac{3 - 0.7 - 0.7}{3.3 + 56.6/101} = 0.41 \text{ mA}$$

$$V_E = 3 - 0.41 \times 3.3 = +1.63 \text{ V}$$

$$V_B = V_E - 0.7 = +0.93 \text{ V}$$

$$V_C = -3 + 5.1 \times 0.41 \times \frac{100}{101} = -0.93 \text{ V}$$

