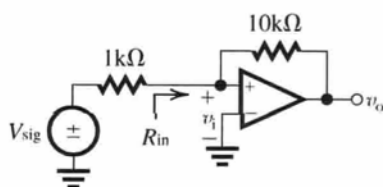


**9.56**

$$R_{in} = \frac{R}{1 - \text{Gain}} = \frac{100 \text{ k}\Omega}{1 - 0.9} = 1000 \text{ k}\Omega = 1 \text{ M}\Omega$$

**Ex: 9.15**



Using Miller's theorem we have

$$R_{in} = \frac{10 \text{ k}\Omega}{A + 1}, V_i = \frac{R_{in}}{R_{in} + 1 \text{ k}\Omega} V_{sig} \text{ and}$$

$$V_o = -AV_i$$

Assuming  $V_{sig} = 1 \text{ V}$  we have

A(V/V)	$R_{in}(\Omega)$	$V_i(\text{mV})$	$V_o(\text{V})$	$V_o/V_{sig}$ $\left(\frac{\text{V}}{\text{V}}\right)$
10	909	476	4.76	4.76
100	99	90	-9	-9
1000	9.99	9.9	-9.9	-9.9
10000	1	0.999	-9.99	-9.99