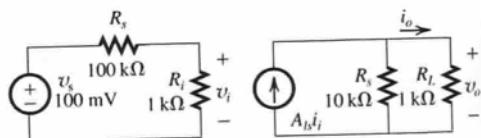


1.53



$$(a) \text{ Current gain} = \frac{i_o}{i_i}$$

$$= A_{is} \frac{R_o}{R_o + R_L}$$

$$= 100 \frac{10}{11}$$

$$= 90.9 \frac{\text{A}}{\text{A}} = 39.2 \text{ dB}$$

$$(b) \text{ Voltage gain} = \frac{v_o}{v_s}$$

$$= \frac{i_o}{i_i} \frac{R_S}{R_S + R_i}$$

$$= 90.9 \times \frac{1}{101}$$

$$= 0.9 \text{ V/V} = -0.9 \text{ dB}$$

$$(c) \text{ Power gain} = A_P = \frac{v_o i_o}{v_s i_i}$$

$$= 0.9 \times 90.9$$

$$= 81.8 \text{ W/W} = 19.1 \text{ dB}$$

Ex: 1.12

$$v_o = 1 \times \frac{10}{10^6 + 10} \approx 10^{-5} \text{ V} = 10 \mu\text{V}$$

$$P_L = v_o^2 / R_L = \frac{(10 \times 10^{-6})^2}{10} = 10^{-11} \text{ W}$$

With the buffer amplifier:

$$\begin{aligned} v_o &= 1 \times \frac{R_i}{R_i + R_S} \times A_{vo} \times \frac{R_L}{R_L + R_o} \\ &= 1 \times \frac{1}{1+1} \times 1 \times \frac{10}{10+10} = 0.25 \text{ V} \end{aligned}$$

$$P_L = \frac{v_o^2}{R_L} = \frac{0.25^2}{10} = 6.25 \text{ mW}$$

$$\begin{aligned} \text{Voltage gain} &= \frac{v_o}{v_s} = \frac{0.25 \text{ V}}{1 \text{ V}} = 0.25 \text{ V/V} \\ &= -12 \text{ dB} \end{aligned}$$

$$\text{Power gain } (A_p) \equiv \frac{P_L}{P_i}$$

where $P_L = 6.25 \text{ mW}$ and $P_i = v_i i_1$,

$v_i = 0.5 \text{ V}$ and

$$i_i = \frac{1 \text{ V}}{1 \text{ M}\Omega + 1 \text{ M}\Omega} = 0.5 \mu\text{A}$$

Thus,


$$P_i = 0.5 \times 0.5 = 0.25 \mu\text{W}$$

and,

$$A_p = \frac{6.25 \times 10^{-3}}{0.25 \times 10^{-6}} = 25 \times 10^3$$

$$10 \log A_p = 44 \text{ dB}$$

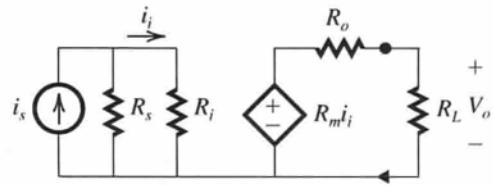Ex: 1.20 Using transresistance circuit model the circuit will be



$$\frac{i_i}{i_s} = \frac{R_s}{R_i + R_s}$$

$$V_o = R_m i_i \times \frac{R_L}{R_L + R_o}$$

$$\frac{V_o}{i_i} = R_m \frac{R_L}{R_L + R_o}$$

$$\begin{aligned} \text{Now } \frac{V_o}{i_s} &= \frac{V_o}{i_i} \times \frac{i_i}{i_s} = R_m \frac{R_L}{R_L + R_o} \times \frac{R_s}{R_i + R_s} \\ &= R_m \frac{R_s}{R_s + R_i} \times \frac{R_L}{R_L + R_o} \end{aligned}$$