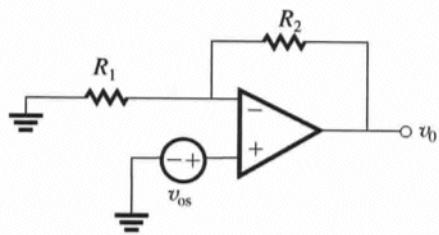


**2.94**

Inverting configuration



$$v_o = v_{os} \left( 1 + \frac{R_2}{R_1} \right)$$

$$-0.4 = v_{os} \left( 1 + \frac{100}{1} \right)$$

$$v_{os} \approx 4 \text{ mV}$$

**2.96**

Input offset voltage = 5 mV

Output dc offset voltage =

5 mV × closed loop gain

$$= 5 \text{ mV} \times 1000$$

$$= 5 \text{ V}$$

The maximum amplifier of an input sinusoid that results in an output peak amplifier of  $13 - 5 = 8 \text{ V}$  is given by:

$$v_i = \frac{8}{1000} = 8 \text{ mV}$$

If amplifier is capacitively coupled then

$$v_{i\max} = \frac{13}{1000} = 13 \text{ mV}$$