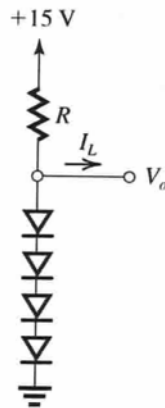


**Ex: 4.15**



a. In this problem  $\frac{\Delta V_o}{\Delta i_L} = \frac{20 \text{ mV}}{1 \text{ mA}} = 20 \Omega$

$\therefore$  Total small signal resistance of the four diodes  
=  $20 \Omega$

$\therefore$  For each diode  $r_d = \frac{20}{4} = 5 \Omega$

But  $r_d = \frac{V_T}{I_D} \Rightarrow 5 = \frac{25 \text{ mV}}{I_D}$

$\therefore I_D = 5 \text{ mA}$

and  $R = \frac{15 - 3}{5 \text{ mA}} = 2.4 \text{ k}\Omega$

b. For  $V_o = 3 \text{ V}$ , voltage drop across each

diode =  $\frac{3}{4} = 0.75 \text{ V}$

$$i_D = I_S e^{v/V_T}$$

$$I_S = \frac{i_D}{e^{v/V_T}} = \frac{5}{e^{0.75/25 \times 10^{-3}}} = 4.7 \times 10^{-16} \text{ A}$$

c. If  $i_D = 5 - i_L = 5 - 1 = 4 \text{ mA}$

Across each diode the voltage drop is

$$V_D = V_T \ln\left(\frac{I_D}{I_S}\right)$$

$$= 25 \times 10^{-3} \times \ln\left(\frac{4 \times 10^{-3}}{4.7 \times 10^{-16}}\right)$$

$$= 0.7443 \text{ V}$$


Voltage drop across 4 diodes

$$= 4 \times 0.7443 = 2.977 \text{ V}$$

so change in  $V_o = 3 - 2.977 = 23 \text{ mV}$

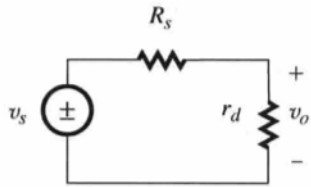**4.46**

The dc current  $I$  flows through the diode giving rise to the diode resistance  $r_d (= \frac{V_T}{I})$  and the Small-Signal equivalent circuit is represented by



$$v_o = v_s \times \frac{r_d}{r_d + R_s} = v_s \frac{V_T/I}{\frac{V_T}{I} + R_s}$$

$$= v_s \frac{V_T}{V_T + IR_s}$$

$$\text{Now } v_o = 5 \text{ mV} \times \frac{25 \text{ mV}}{25 \text{ mV} + 10^3 I}$$

$$= 0.005 \times \frac{0.025}{0.025 + 10^3 I}$$

$I$	$v_o$
1 mA	0.122 mV
0.1 mA	1.0 mV
1 $\mu$ A	5.0 mV

$$\text{For } v_o = \frac{1}{2} V_s = v_s \times \frac{0.025}{0.025 + 10^3 I}$$

$$\Rightarrow I = 25 \mu\text{A}$$