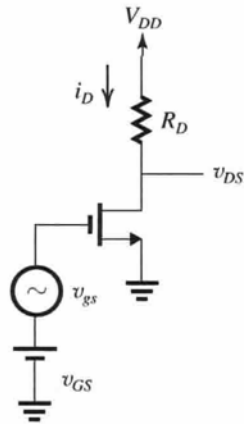


5.71



$$V_t = 0.4 \text{ V}, k_n = 4 \text{ mA/V}^2$$

$$V_{GS} = 0.65 \text{ V}, V_{DD} = 1.8 \text{ V}$$

$$R_D = 8 \text{ k}\Omega \quad (V_{ov} = 0.25 \text{ V})$$

$$(a) I_D = \frac{1}{2} k_n V_{ov}^2 = 125 \text{ }\mu\text{A}$$

$$V_{DS} = V_{DD} - I_D R_D = 0.8 \text{ V}$$

$$(b) g_m = k_n V_{ov} = 1 \text{ mS}$$

$$(c) A_v = -g_m R_D = -8.0$$

$$(d) \text{ for } \lambda = 0.1 \text{ V}^{-1}$$

$$V_0 \cong \frac{1}{\lambda I_D} = 80 \text{ k}\Omega$$

$$A_v = -g_m (r_0 \parallel R_D) = -7.3$$

$$5.72 |v_o| = 0.5 \text{ V, peak} \quad R_D = 50 \text{ k}\Omega$$

$$V_{DD} = 1.8 \text{ V}, \quad |A_v| = 5$$

$$g_m = \frac{A_v}{R_D} = 100 \text{ }\mu\text{S} = k_n V_{ov} = \frac{2I_D}{V_{ov}}$$

$$5.79 \quad V_t = 1 \text{ V}, k'_n = \frac{W}{L} = 2 \text{ mA/V}^2$$

$$(a) \text{ dc analysis } V_G = \frac{5}{15} 15 \text{ V} = 5 \text{ V}, \text{ assume}$$

$$I_D = 1 \text{ mA}$$

$$V_S = 3 \text{ V}, V_{GS} = 2 \text{ V}, V_{OV} = 1 \text{ V}.$$


$$I_D = \frac{1}{2} k'_n V_{OV}^2 = 1 \text{ mA (check)}$$

$$V_D = V_{DD} - I_D R_D = 7.5 \text{ V}.$$

$$(b) r_0 = \frac{V_A}{I_D} = \frac{100 \text{ V}}{1 \text{ mA}} = 100 \text{ k}\Omega$$

$$g_m = \sqrt{2k'_n I_D} = 2 \text{ mS}$$

(c)

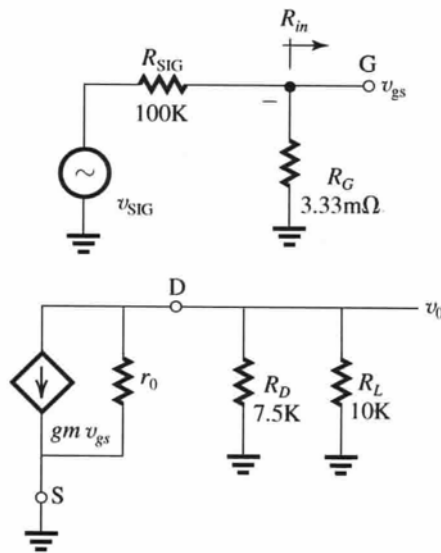

$$(d) R_{in} = R_G = 3.33 \text{ M}\Omega$$

$$\frac{v_{gs}}{v_{sig}} = \frac{R_{in}}{R_{sig} + R_{in}} = 0.97$$

$$\frac{v_0}{v_{gs}} = -g_m (r_0 \parallel R_D \parallel R_L) = -8.2$$

$$\frac{v_0}{v_{sig}} = -8.0$$