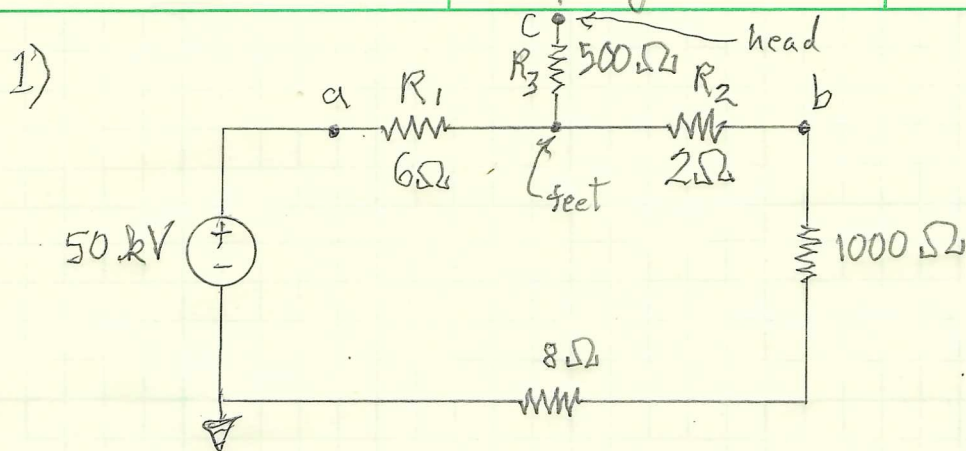




a) Since no current passes through the bird, the voltage at its head is the same as at its feet.

Total resistance seen by source is $6 + 2 + 1000 + 8 \Omega = 1016 \Omega$


Current that flows is $\frac{50kV}{1016 \Omega} = 49.213 A$

Voltage drop across 6Ω resistor $= (6 \Omega)(49.213 A) = 295.28 V$

Therefore voltage at bird's feet & head is $50,000 - 295.28 = \underline{\underline{49,704.72 V}}$

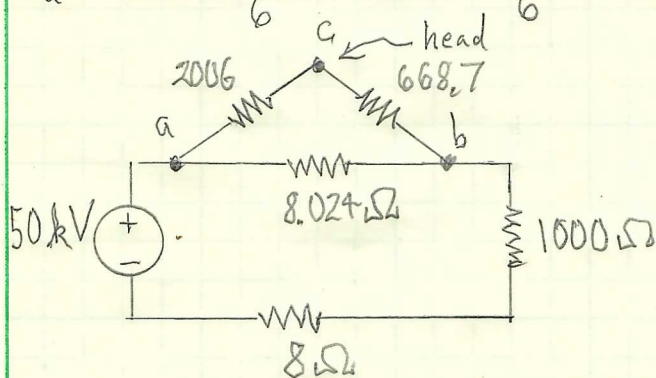b) Y-to- Δ transformation:

$$R_a = \frac{6(2) + 2(500) + 500(6)}{6} = \frac{4012}{6} = 668.7 \Omega, R_b = \frac{4012}{2} = 2006 \Omega, R_c = \frac{4012}{500} = 8.024 \Omega$$



Resistance between a & b is still 8Ω :

$$(R_a + R_b) \parallel R_c = \frac{(2674.6)(8.024)}{2674.6 + 8.024} = 8 \Omega$$

Thus, $49.213 A$ still flow from source and through 1000Ω & 8Ω ,

$$\Rightarrow \text{Voltage } b = (49.213 A)(1000 \Omega + 8 \Omega) = 49,606.3 V$$


c) Voltage drop from a to b is $50,000 - 49,606.3 = 393.7 V$

So, current through resistors a & b $= \frac{393.7 V}{(2006 + 668.7) \Omega} = 0.1472 A$

$$\Rightarrow \text{Voltage at bird's head} = 50,000 - (2006 \Omega)(0.1472 A) = \underline{\underline{49,704.72 V}}$$

Q. E. D.

2) a)

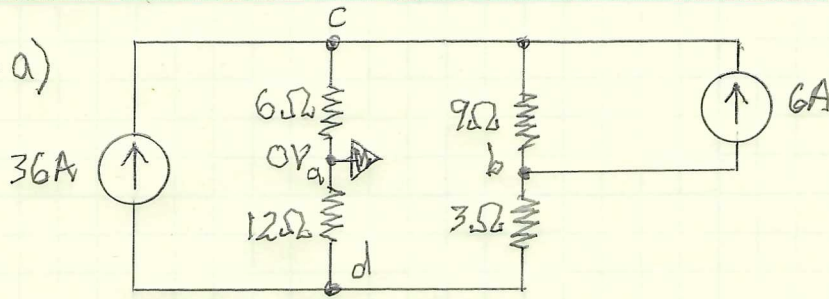

$$\text{At } b: \frac{V_b - V_d}{3} + \frac{V_b - V_c}{9} + 6 = 0 \Rightarrow \left(\frac{1}{3} + \frac{1}{9}\right)V_b - \frac{1}{9}V_c - \frac{1}{3}V_d = -6$$

$$\text{At } c: -36 + \frac{V_c}{6} + \frac{V_c - V_b}{9} - 6 = 0 \Rightarrow -\frac{1}{9}V_b + \left(\frac{1}{6} + \frac{1}{9}\right)V_c = 42$$

$$\text{At } d: 36 + \frac{V_d}{12} + \frac{V_d - V_b}{3} = 0 \Rightarrow -\frac{1}{3}V_b + \left(\frac{1}{12} + \frac{1}{3}\right)V_d = -36$$


$$\text{Using MATLAB: } \underline{V_b = -135V}, \quad \underline{V_c = 97.2V}, \quad \underline{V_d = -194.4V}$$

```
g = [(1/3+1/9), -1/9, -1/3;
      -1/9, (1/6+1/9), 0;
      -1/3, 0, (1/12+1/3)];
v = g \ [-6; 42; -36]
```

```
v = 3x1
10^2 x
-1.3500000000000000
 0.9720000000000000
-1.9440000000000001
```

(continued)

2) b)

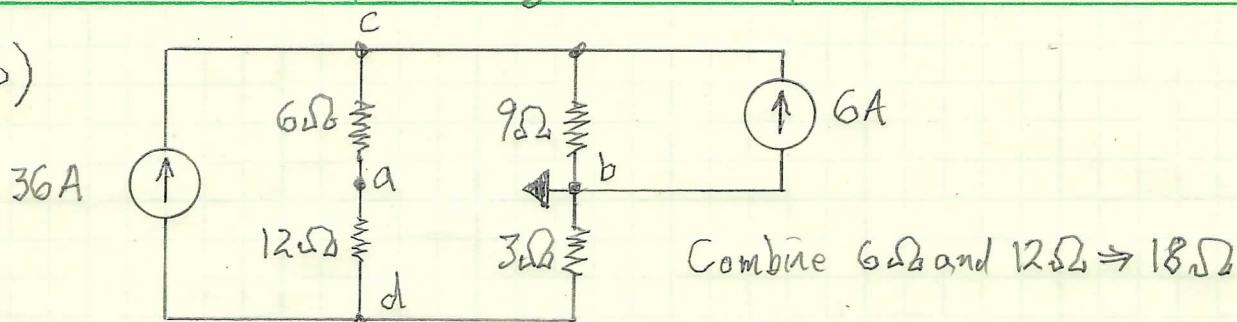

$$\text{At } c: -36 + \frac{V_c - V_d}{18} + \frac{V_c}{9} - 6 = 0 \Rightarrow \left(\frac{1}{18} + \frac{1}{9}\right)V_c - \frac{1}{18}V_d = 42$$

$$\text{At } d: 36 + \frac{V_d - V_c}{18} + \frac{V_d}{3} = 0 \Rightarrow -\frac{1}{18}V_c + \left(\frac{1}{18} + \frac{1}{3}\right)V_d = -36$$

Using MATLAB: $V_c = 232.2V$, $V_d = -59.4V$

```
g = [(1/18+1/9), -1/18;
     -1/18, (1/18+1/3)];
v = g \ [42; -36]
```

```
v = 2x1
10^2 x
 2.3220000000000000
-0.5940000000000000
```


Use voltage division to find V_a .

$$V_a = \underbrace{\frac{12\Omega}{12\Omega + 6\Omega}}_{\text{voltage across } 12\Omega \text{ resistor}} (V_c - V_d) + V_d = \underline{\underline{135V}}$$

potential on which 12Ω resistor sits

Node voltages change based on placement of ground, but voltage across elements is independent of ground location.

3)

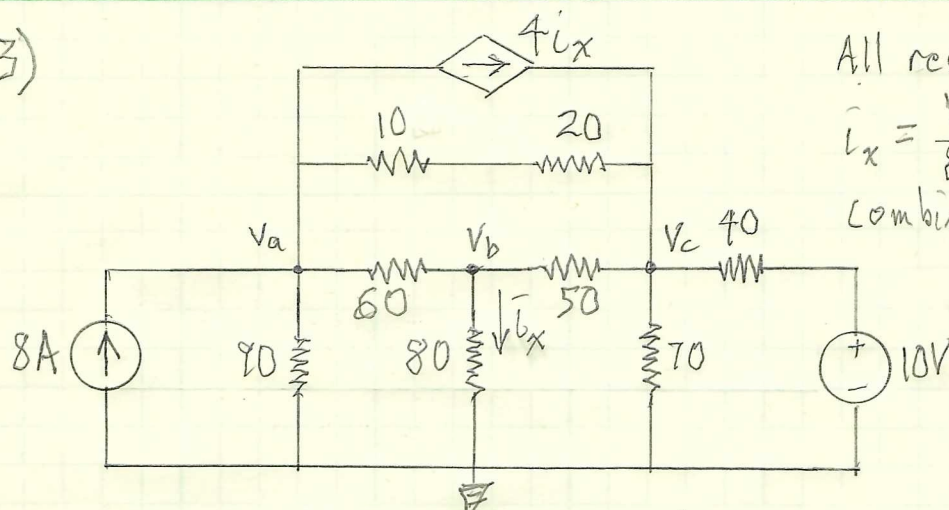

All resistances in ohms.

$$i_x = \frac{V_b}{80}$$

Combine $10 \parallel 20 \Omega$ resistors = 30Ω .

$$\text{At } a: -8 + \frac{V_a}{90} + \frac{V_a - V_b}{60} + \frac{V_a - V_c}{30} + 4 \frac{V_b}{80} = 0$$

$$\Rightarrow \left(\frac{1}{90} + \frac{1}{60} + \frac{1}{30}\right)V_a + \left(-\frac{1}{60} + \frac{1}{20}\right)V_b + \left(-\frac{1}{30}\right)V_c = 8$$

$$\text{At } b: \frac{V_b - V_a}{60} + \frac{V_b}{80} + \frac{V_b - V_c}{50} = 0 \Rightarrow \left(-\frac{1}{60}\right)V_a + \left(\frac{1}{60} + \frac{1}{80} + \frac{1}{50}\right)V_b + \left(-\frac{1}{50}\right)V_c = 0$$

$$\text{At } c: -4 \frac{V_b}{80} + \frac{V_c - V_a}{30} + \frac{V_c - V_b}{50} + \frac{V_c}{70} + \frac{V_c - 10}{40} = 0$$


$$\Rightarrow \left(-\frac{1}{30}\right)V_a + \left(-\frac{1}{20} - \frac{1}{50}\right)V_b + \left(\frac{1}{30} + \frac{1}{50} + \frac{1}{70} + \frac{1}{40}\right)V_c = \frac{1}{4}$$

$$\begin{bmatrix} \left(\frac{1}{90} + \frac{1}{60} + \frac{1}{30}\right) & \left(-\frac{1}{60} + \frac{1}{20}\right) & \left(-\frac{1}{30}\right) \\ \left(-\frac{1}{60}\right) & \left(\frac{1}{60} + \frac{1}{80} + \frac{1}{50}\right) & \left(-\frac{1}{50}\right) \\ \left(-\frac{1}{30}\right) & \left(-\frac{1}{20} - \frac{1}{50}\right) & \left(\frac{1}{30} + \frac{1}{50} + \frac{1}{70} + \frac{1}{40}\right) \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 8 \\ 0 \\ \frac{1}{4} \end{bmatrix}$$

$$\Rightarrow V_a = 147.34V, \quad V_b = 104.85V, \quad V_c = 134.97V$$

$$\underline{\underline{i_x = \frac{V_b}{80 \Omega} = 1.311A}}$$

4)

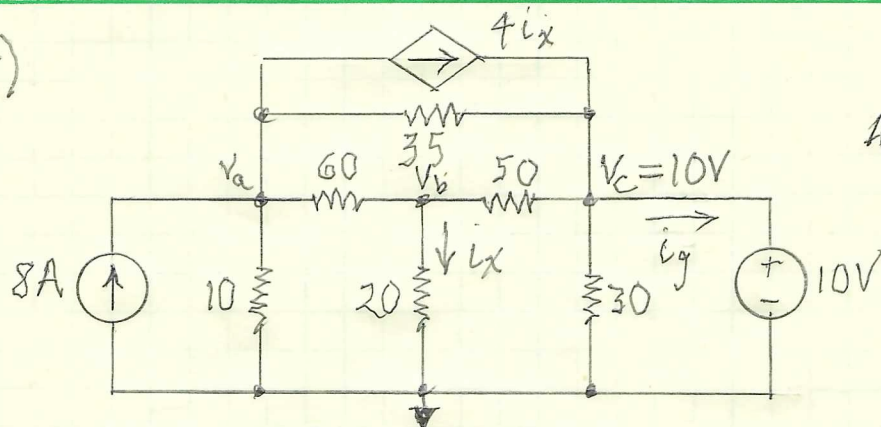

$$60 \parallel 84 = 35 \Omega$$

All resistances in ohms

$$i_x = \frac{V_b}{20}$$

$$\text{At } a: -8 + \frac{V_a}{10} + \frac{V_a - V_b}{60} + \frac{V_a - 10}{35} + 4 \frac{V_b}{20} = 0 \Rightarrow \left(\frac{1}{10} + \frac{1}{60} + \frac{1}{35}\right)V_a + \left(\frac{1}{5} - \frac{1}{60}\right)V_b = 8 + \frac{2}{7}$$

$$\text{At } b: \frac{V_b - V_a}{60} + \frac{V_b}{20} + \frac{V_b - 10}{50} = 0 \Rightarrow -\frac{1}{60}V_a + \left(\frac{1}{60} + \frac{1}{20} + \frac{1}{50}\right)V_b = \frac{1}{5}$$

$$\text{Using MATLAB: } V_a = 43.562 \text{ V}, \quad V_b = 10.685 \text{ V}$$

```
g = [(1/10+1/60+1/35), (1/5-1/60);
     -1/60,              (1/60+1/20+1/50)];
v = g \ [8 + 2/7; 1/5]
```

```
v = 2x1
    43.561643835616444
    10.684931506849313
```

$$i_x = \frac{V_b}{20} = 0.534 \text{ A}$$

$$\text{KCL at } c: -4 \frac{V_b}{20} + \frac{10 - V_a}{35} + \frac{10 - V_b}{50} + \frac{10}{30} + i_g = 0$$

$$\Rightarrow i_g = -\left(\frac{1}{35} + \frac{1}{50} + \frac{1}{30}\right)10 + \frac{1}{35}V_a + \left(\frac{1}{5} + \frac{1}{50}\right)V_b$$

$$\Rightarrow \underline{i_g = 2.776 \text{ A}}$$