
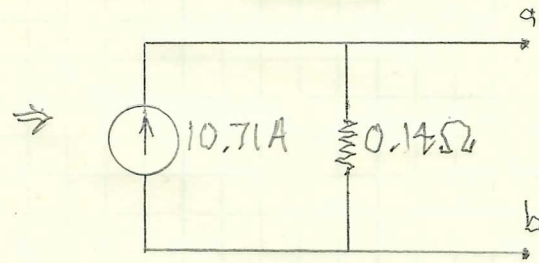


$$1) a) I_{sc} = I_N = \frac{1.5V}{0.14\Omega} = \underline{\underline{10.71A}}$$
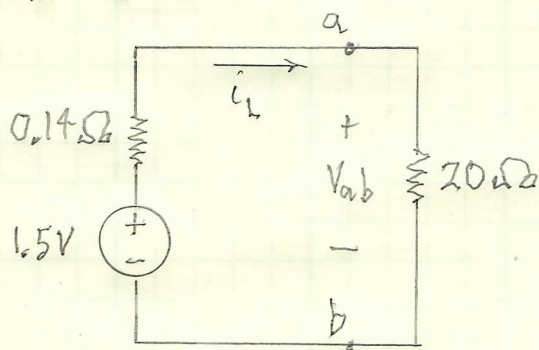
$$R_N = R_{th} = \underline{\underline{0.14\Omega}}$$



b) $R_L = 20\Omega$, Use Thévenin circuit to obtain values.



Voltage division:

$$V_{ab} = \frac{20}{20 + 0.14} 1.5V = \underline{\underline{1.48956V}}$$

$$i_L = \frac{V_{ab}}{20\Omega} = \underline{\underline{0.07448A = 74.48mA}}$$


or, could have used Norton circuit.

$$R_{eq} = 20\Omega \parallel 0.14\Omega = 0.13903\Omega$$

$$\Rightarrow V_{ab} = I_N R_{eq} = \underline{\underline{1.48956V}}$$

Same as above,
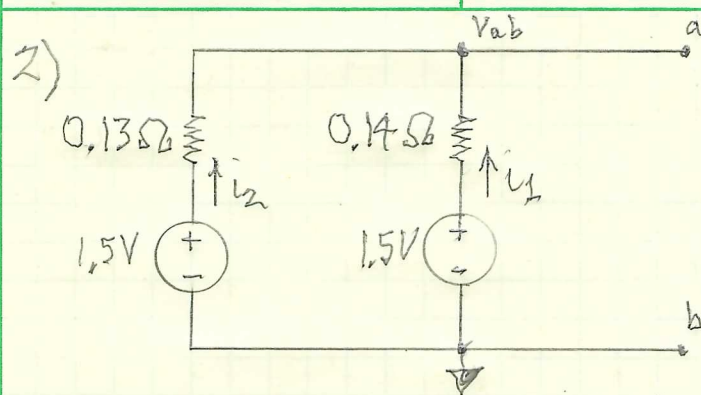
$$i_L = \frac{R_{eq}}{20\Omega} I_N = \underline{\underline{74.48mA}}$$





a) With open circuit, apply KCL to top node:

$$\frac{V_{ab} - 1.5}{0.13} + \frac{V_{ab} - 1.5}{0.14} = 0 \Rightarrow \left(\frac{1}{0.13} + \frac{1}{0.14}\right) V_{ab} = \left(\frac{1}{0.13} + \frac{1}{0.14}\right) 1.5V \Rightarrow \underline{V_{ab} = 1.5V = V_{th}}$$

Because there are only independent sources, deactivate and find remaining resistance.

$$R_{eq} = 0.13 \parallel 0.14 = 0.06741\Omega = \underline{67.41m\Omega = R_{th}}$$

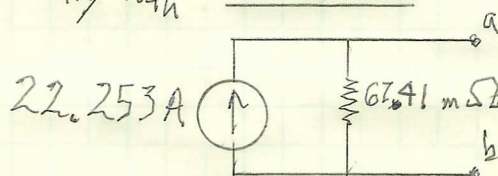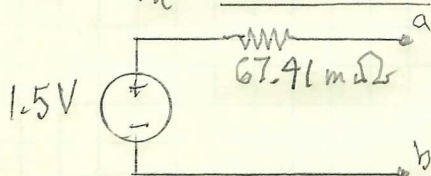b) $R_N = R_{th} = \underline{67.41m\Omega}$, $I_N = V_{th}/R_{th} = \underline{22.253A}$




c) Voltage division: $V_{ab} = \frac{20}{20 + 0.06741} 1.5V = \underline{1.495V = V_L}$

$$i_L = V_L / 20\Omega = 0.07478A = \underline{74.75mA = i_L}$$

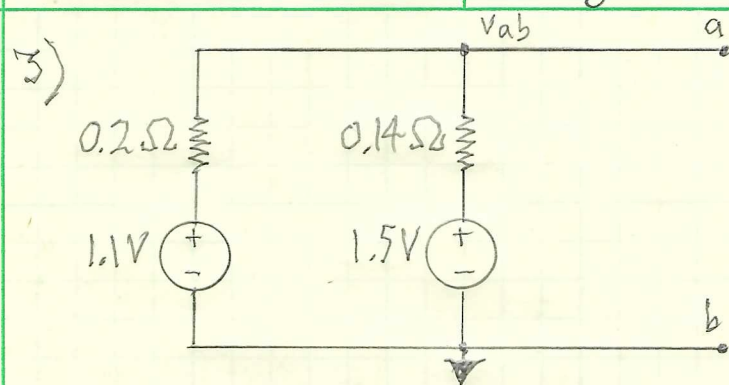d) $i_2 = \frac{1.5V - V_L}{0.13\Omega} = 0.03876A = \underline{38.76mA}$

$$i_1 = \frac{1.5V - V_L}{0.14\Omega} = 0.03599A = \underline{35.99mA}$$

Note that the voltage across and the current through the load are almost identical to the single-battery case. But, the current through the batteries is now approximately half of what it was before. Thus, the two batteries are each delivering about half the power that a single battery had to deliver.




a) With open circuit, apply KCL to top node:

$$\frac{V_{ab} - 1.1}{0.2} + \frac{V_{ab} - 1.5}{0.14} = 0 \Rightarrow \left(\frac{1}{0.2} + \frac{1}{0.14}\right)V_{ab} = \frac{1.1}{0.2} + \frac{1.5}{0.14} \Rightarrow \underline{V_{ab} = 1.335V = V_{th}}$$

Because there are only independent sources, deactivate them and find remaining resistance: $R_{eq} = 0.2 \parallel 0.14 = 0.08235\Omega = 82.35\text{ m}\Omega = R_{th}$

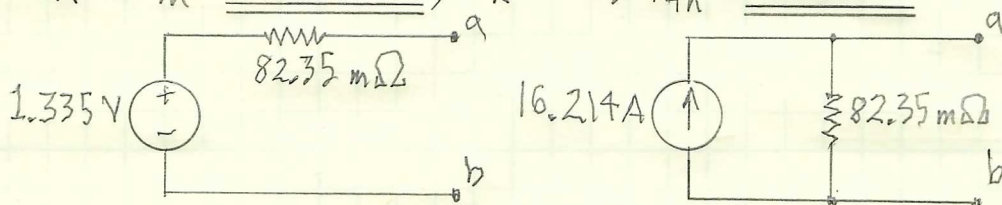b) $R_N = R_{th} = 82.35\text{ m}\Omega$, $I_N = V_{th}/R_{th} = 16.214\text{ A}$



c) Voltage division: $V_{ab} = \frac{20}{20 + 0.08235} 1.335V = \underline{1.3298V = V_L}$

$$i_L = V_L / 20\Omega = 0.06649\text{ A} = \underline{66.49\text{ mA} = i_L}$$


$$i_2 = \frac{1.1V - V_L}{0.2} = \underline{-1.149\text{ A}}$$

$$i_1 = \frac{1.5 - V_L}{0.14} = \underline{1.216\text{ A}}$$

Note that the voltage across the load hasn't changed much from when there were two fresh batteries. But there is a huge change in the currents flowing through the batteries. The current through Battery 1 has now increase by a factor of more than 33 from when it was in parallel with another fresh battery.

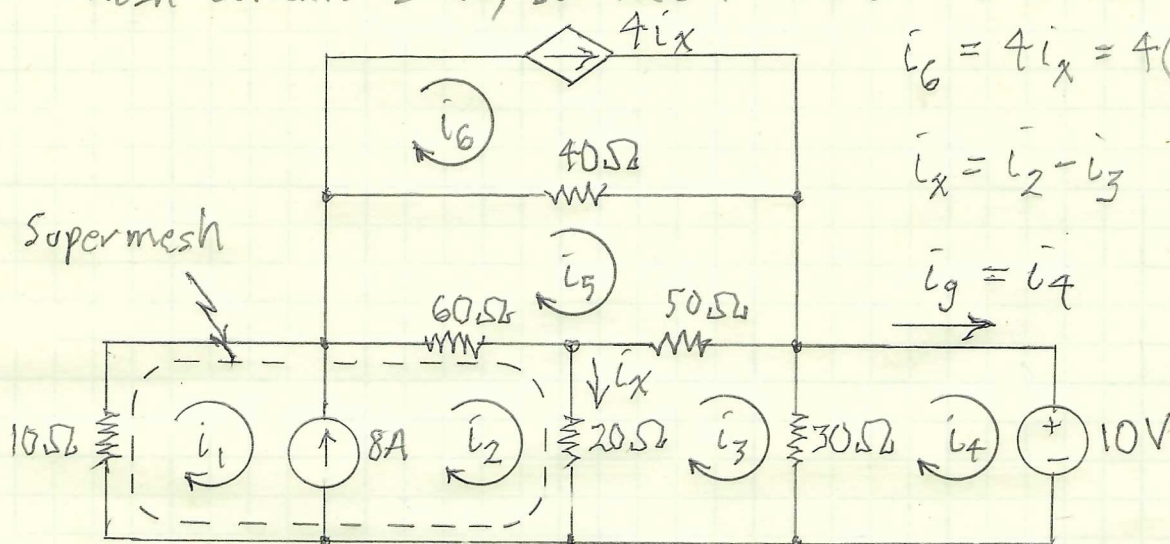4) Parallel resistors: $72\Omega \parallel 90\Omega = 40\Omega$

Could swap $8A$ & 10Ω resistor, which would dictate one of the mesh currents is $8A$, but leave it where it is and use super mesh.



$$\text{Supermesh: } 10\bar{i}_1 + 60(\bar{i}_2 - \bar{i}_5) + 20(\bar{i}_2 - \bar{i}_3) = 0 \Rightarrow 10\bar{i}_1 + (60+20)\bar{i}_2 - 20\bar{i}_3 - 60\bar{i}_5 = 0$$

$$\text{Mesh 3: } 20(i_3 - i_2) + 50(i_3 - i_5) + 30(i_3 - i_4) = 0 \Rightarrow -20i_2 + (20 + 50 + 30)i_3 - 30i_4 - 50i_5 = 0$$

$$\text{Mesh 4: } 30(i_4 - i_3) + 10 = 0 \Rightarrow -30i_3 + 30i_4 = -10$$

$$\text{Mesh 5: } 40(\bar{i}_5 - 4[\bar{i}_2 - \bar{i}_3]) + 50(\bar{i}_5 - \bar{i}_3) + 60(\bar{i}_5 - \bar{i}_2) = 0$$

$$\Rightarrow (-160-60)i_2 + (160-50)i_3 + (40+50+60)i_5 = 0$$

Constraint equation: $\bar{i}_2 = 8 + \bar{i}_1 \Rightarrow -\bar{i}_1 + \bar{i}_2 = 8$

Using MATLAB:

```
r = [10, (60+20), -20, 0, -60;
      0, -20, (20+50+30), -30, -50;
      0, 0, -30, 30, 0;
      0, (-160-60), (160-50), 0, (40+50+60);
      -1, 1, 0, 0, 0];
is = r \ [0; 0; -10; 0; 8]
```

is = 5x1

$-4.423913043478268 \approx l_1$

$3.576086956521739 \approx l_2$

$3.035326086956521 \approx l_3$

$2.701992753623188 \approx l_4 = l_9$

3.019021739130434

$$i_x = i_2 - i_3 = 3.576 - 3.035 = 0.541 \text{ A}$$

$$\underline{\underline{I_g = 2.702 A}}$$