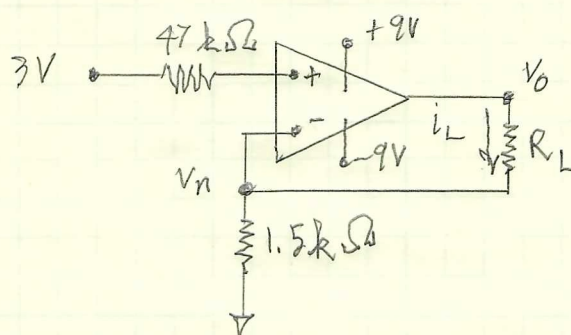


1) 5.39)



3V source tied to V_p . So $V_p = 3V$.
In linear region $V_n = V_p = 3V$.

a) Voltage division: $V_n = 3V = \frac{1.5k\Omega}{R_L + 1.5k\Omega} V_o$

Using $R_L = 2.5k\Omega \Rightarrow V_o = \frac{4}{1.5} 3V = 8V \Rightarrow i_L = \frac{8V - 3V}{2.5k} = \underline{\underline{2mA}}$

b) Output voltage is bound by $\pm 9V$. (Because input voltage is positive, the $-9V$ limit isn't a factor.)

Voltage division when $V_o = 9V$: $V_n = 3V = \frac{1.5k}{R_L + 1.5k} 9V$

$\Rightarrow R_L + 1.5k = 4.5k \Rightarrow R_{Lmax} = \underline{\underline{3k\Omega}}$

c) Beyond $R_L = 3k\Omega$, V_o will be pegged at $9V$. As R_L increases, more of this voltage, i.e., more of the $9V$, would be dropped across R_L and less across the $1.5k\Omega$ resistor. Thus, V_n would drop below $3V$, but the op-amp couldn't do anything more to try to bring V_n and V_p back together.

d) See plot on next page.

EE 261
1) d) (continued)


Spring 2025

Homework #7

2


```
% N&R Prob. 5.39(d).  
% Create resistances between 0 and 6.5k, but will leave "k" understood.  
rl = linspace(0, 6.5, 351);  
% Current for R_L less than 3k is a constant 2 mA.  
il = (2) * (rl < 3);  
% Add current for R_L greater than 3k when output fixed at 9 V.  
il = il + (9 ./ (rl + 1.5)) .* ~(rl < 3);
```
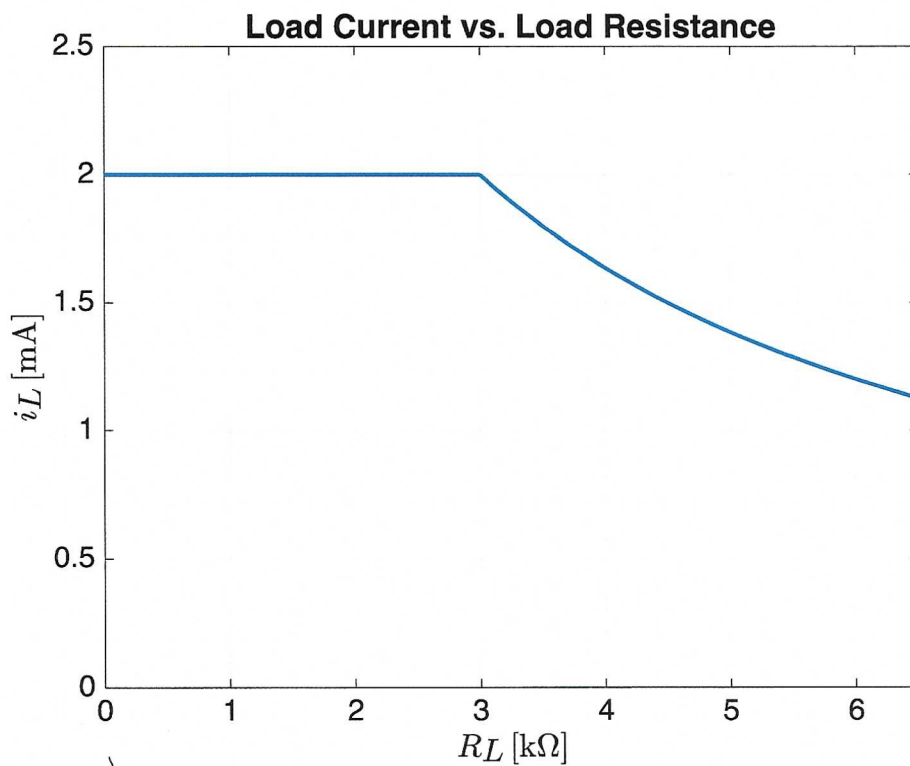
```
plot(rl, il, 'LineWidth', 2)  
grid on  
set(gca, 'FontSize', 16)  
xlabel('$R_L$ [k$\Omega$]', 'Interpreter', 'latex')  
ylabel('$i_L$ [mA]', 'Interpreter', 'latex')  
title('Load Current vs. Load Resistance')  
axis([0 6.5 0 2.5])
```



Circuit acts
like a constant
current source for
loads in this range.

2) 5.42

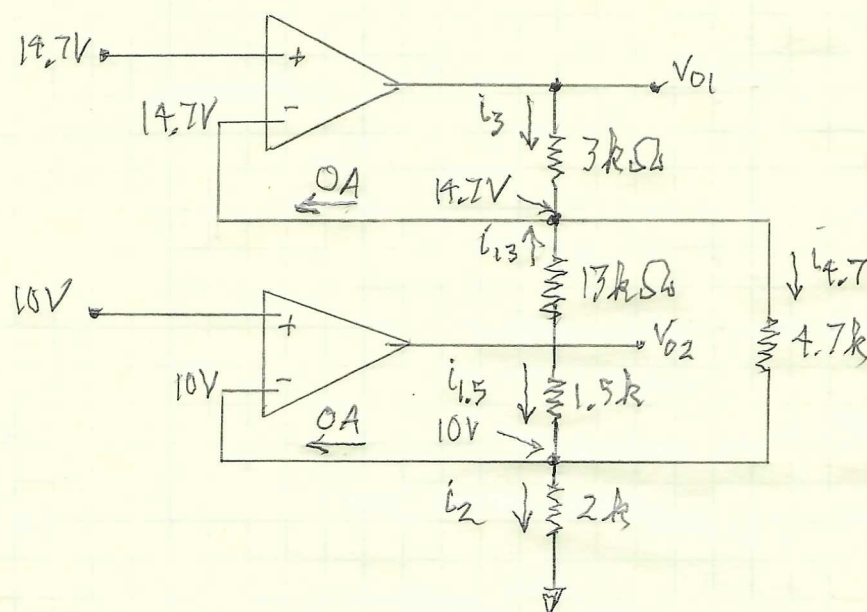

$$i_2 = 10V / 2000 = 5mA, \quad i_{4.7} = (14.7 - 10)V / 4700 = 1mA$$

$$i_{1.5} + i_{4.7} = i_2 \Rightarrow i_{1.5} = i_2 - i_{4.7} = 4mA$$

$$\Rightarrow V_{02} = 10V + i_{1.5} \cdot 1500\Omega = 10 + 6 = \underline{\underline{16V = V_{02}}}$$

$$i_{13} = (V_{02} - 14.7V) / 13000\Omega = 0.1mA$$

$$i_3 + i_{13} = i_{4.7} \Rightarrow i_3 = i_{4.7} - i_{13} = 1mA - 0.1mA = 0.9mA$$

$$\Rightarrow V_{01} = 14.7V + i_3 \cdot 3000\Omega = 14.7 + 2.7 = \underline{\underline{17.4V = V_{01}}}$$

$$3) \quad i(t) = \begin{cases} 10 \text{ A}, & t < 0 \\ 10(t+1)e^{-2t} \text{ A}, & 0 \leq t \leq 1 \text{ s} \\ 20e^{-2} \text{ A}, & 1 \leq t \end{cases}$$


$$L = 15 \text{ mH}, \quad v(t) = L \frac{di(t)}{dt}$$

$$\Rightarrow v(t) = \begin{cases} 0, & t < 0 \\ 0.15(10e^{-2t} - 20(t+1)e^{-2t}) = -0.15(2t+1)e^{-2t} \text{ V}, & 0 < t < 1 \text{ s} \\ 0, & 1 \leq t \end{cases}$$

The voltage is discontinuous and undefined at $t=0$ and $t=1$,
Plot (optional) is shown on next page.

% EE 261, HW 7, Problem 3

```
t = linspace(-0.5, 1.5, 601);  
  
v0 = zeros(1, length(t));  
v1 = -0.15 * (2 * t + 1) .* exp(-2 * t);  
  
plot(t(t<0), v0(t<0), 'b', 'LineWidth', 2)  
hold on  
plot(t(all([t >= 0; t <= 1])), v1(all([t >= 0; t <= 1])), ...  
     'b', 'LineWidth', 2)  
plot(t(t>1), v0(t>1), 'b', 'LineWidth', 2)  
xlabel('$t$', 'Interpreter', 'latex')  
ylabel('$v(t)$', 'Interpreter', 'latex')  
grid on  
axis([-0.5 1.5 -0.16 0.01])  
set(gca, 'FontSize', 18)
```

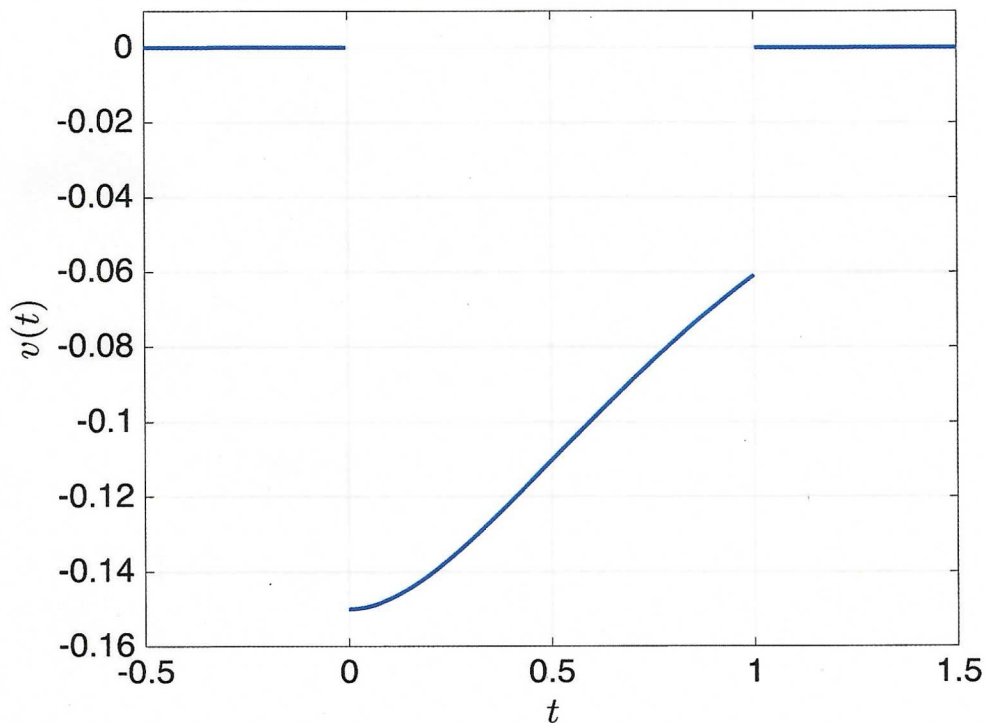

4) $C = 100 \mu F = 10^{-4} F$. Initially uncharged.

$$V_c(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + V_c(t_0)$$

For $t < 0$, $V_c(t) = 10^4 \int_{-\infty}^t 0 d\tau + V_c(-\infty) = 0V$

For $0 < t < 1s$, $V_c(t) = 10^4 \int_0^t (-5 \times 10^{-4}) d\tau + V_c(0) = -5\tau \Big|_0^t + 0 = -5t V$

Note: $V_c(1) = -5V$

For $1 < t < 2s$, $V_c(t) = 10^4 \int_1^t 0 d\tau + V_c(1) = 0 - 5V = -5V$



Note: $V_c(2) = -5V$

For $2 < t < 3s$, $V_c(t) = 10^4 \int_2^t (5 \times 10^{-4}) \tau + V_c(2) = 5\tau \Big|_2^t - 5 = 5(t-2) - 5 = 5(t-3) V$


Note: $V_c(3) = 0V$

For $t > 3$, $V_c(t) = 10^4 \int_3^t 0 d\tau + V_c(3) = 0 + 0 = 0$
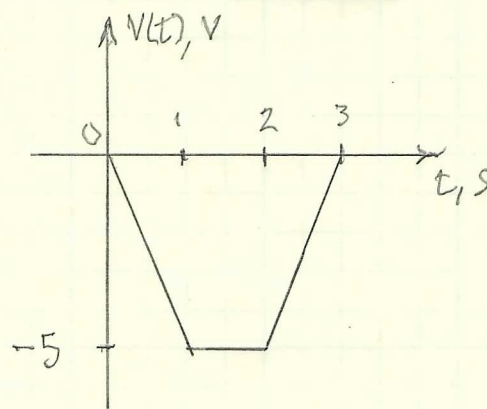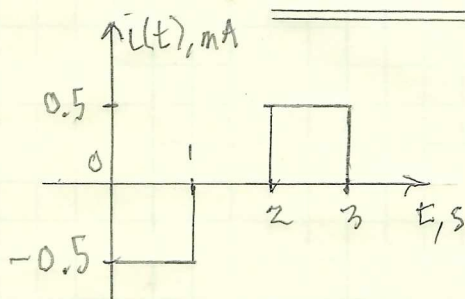
$$\Rightarrow V_c(t) = \begin{cases} 0V & \text{for } t \leq 0 \\ -5tV & \text{for } 0 \leq t \leq 1s \\ -5V & \text{for } 1 \leq t \leq 2s \\ 5(t-3)V & \text{for } 2 \leq t \leq 3s \\ 0 & \text{for } t \geq 3s \end{cases}$$



5)

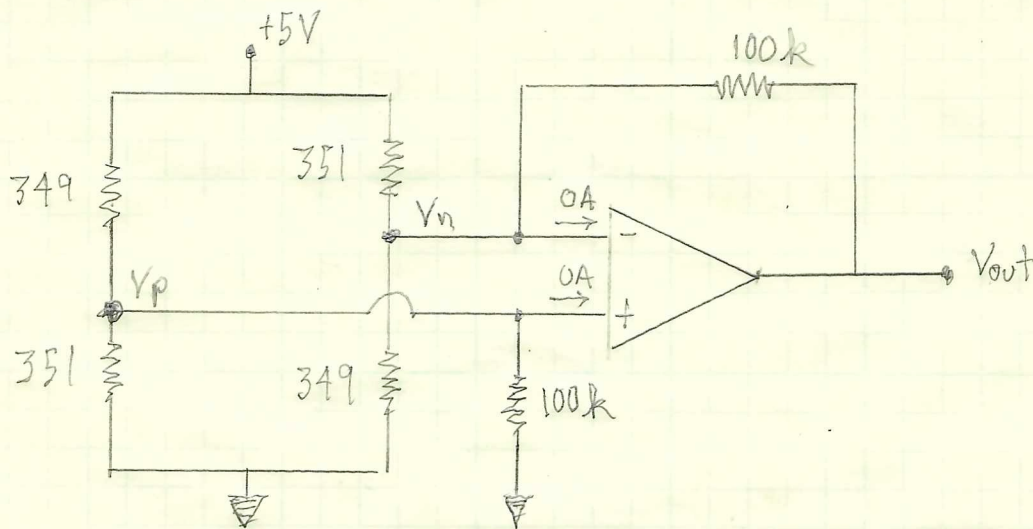

Can obtain voltage at V_p from voltage division. Note that the 351Ω resistor is in parallel with the $100k\Omega$ at non-inverting terminal.

$$351\Omega \parallel 100k\Omega = 349.772\Omega$$

$$\Rightarrow V_p = \frac{349.772}{349 + 349.772} (5V) = 2.50276V = V_n$$

$V_n = V_p$. Now write KCL at inverting terminal.

$$\frac{V_n - 5}{351} + \frac{V_n}{349} + \frac{V_n - V_{out}}{100k} = 0$$

$$\Rightarrow \underline{V_{out}} = 10^5 \left[\frac{V_n - 5}{351} + \frac{V_n}{349} \right] + V_n = \underline{8.163V}$$

Aside: If there is no strain, so that each of the resistors in the bridge (presumably) have a resistance of 350Ω , then the output voltage is zero.