

$$1) \quad v_1(t) = 3 \frac{di_1}{dt} + \frac{di_2}{dt}$$

$$v_2(t) = -4 \frac{di_2}{dt} - \frac{di_1}{dt}$$


$$i_1(t) = 4 \cos(200t) \text{ A} \Rightarrow \frac{di_1}{dt} = -800 \sin(200t) \text{ A/s}$$

$$i_2(t) = 2e^{-150t^2} \text{ A} \Rightarrow \frac{di_2}{dt} = 2(-300t)e^{-150t^2} \text{ A/s}$$

$$\Rightarrow \underline{v_1(t) = -2400 \sin(200t) - 600t e^{-150t^2} \text{ V}}$$

$$\underline{v_2(t) = 2400 e^{-150t^2} + 800 \sin(200t) \text{ V}}$$

2) Prob. 6.39) a)

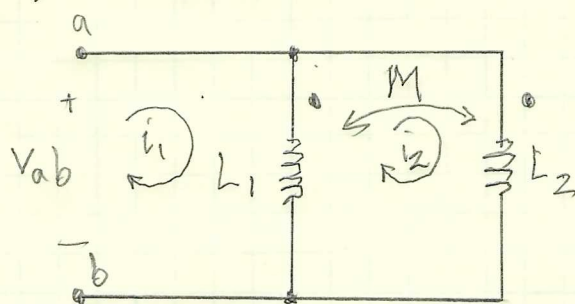

$$\text{Mesh 1: } -V_{ab} + L_1 \frac{d(i_1 - i_2)}{dt} + M \frac{di_2}{dt} = 0 \quad (1)$$

$$\text{Mesh 2: } L_1 \frac{d(i_2 - i_1)}{dt} - M \frac{di_2}{dt} + L_2 \frac{di_2}{dt} + M \frac{d(i_1 - i_2)}{dt} = 0 \quad (2)$$

$$\Rightarrow (L_1 - M + L_2 - M) \frac{di_2}{dt} - (L_1 - M) \frac{di_1}{dt} = 0$$

$$\Rightarrow \frac{di_2}{dt} = \frac{L_1 - M}{L_1 + L_2 - 2M} \frac{di_1}{dt} \quad (3)$$

From (1), we have

$$V_{ab} = L_1 \frac{di_1}{dt} - (L_1 - M) \frac{di_2}{dt}$$

Plugging in (3) yields

$$V_{ab} = L_1 \frac{di_1}{dt} - \frac{(L_1 - M)(L_1 - M)}{L_1 + L_2 - 2M} \frac{di_1}{dt}$$

$$= \left(L_1 - \frac{L_1^2 - 2L_1M + M^2}{L_1 + L_2 - 2M} \right) \frac{di_1}{dt} = \left(\frac{L_1^2 + L_1L_2 - 2L_1M - L_1^2 + 2L_1M - M^2}{L_1 + L_2 - 2M} \right) \frac{di_1}{dt}$$


$$= \left(\frac{L_1L_2 - M^2}{L_1 + L_2 - 2M} \right) \frac{di_1}{dt} = L_{eq} \frac{di_1}{dt}$$

$$\Rightarrow \underline{\underline{L_{eq} = \frac{L_1L_2 - M^2}{L_1 + L_2 - 2M}}}$$

Q.E.D.

(Alternative solution on next page.)

2) (alternate) Prob. 6.39) a)

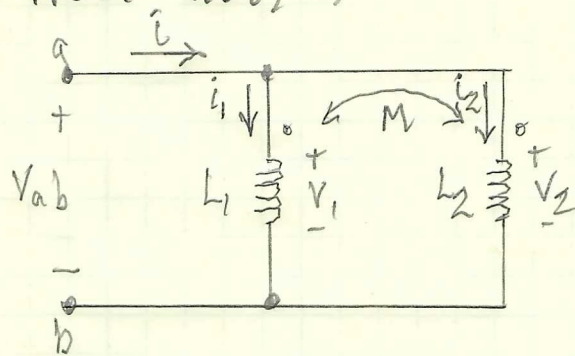

$$\bar{i} = i_1 + i_2$$

All voltages are in parallel:

$$V_{ab} = L_{eq} \frac{d\bar{i}}{dt} = L_{eq} \frac{d(i_1 + i_2)}{dt} = V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} = V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$\text{Regroup terms: } (L_1 - M) \frac{di_1}{dt} = (L_2 - M) \frac{di_2}{dt}$$

$$\Rightarrow \frac{di_1}{dt} = \frac{L_2 - M}{L_1 - M} \frac{di_2}{dt}$$


$$\begin{aligned} \text{Thus } V_{ab} &= L_{eq} \left(\frac{di_1}{dt} + \frac{di_2}{dt} \right) = L_{eq} \left(\frac{L_2 - M}{L_1 - M} + 1 \right) \frac{di_2}{dt} = L_{eq} \left(\frac{L_1 + L_2 - 2M}{L_1 - M} \right) \frac{di_2}{dt} \\ &= V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} = \left(L_2 + M \frac{L_2 - M}{L_1 - M} \right) \frac{di_2}{dt} = \left(\frac{L_1 L_2 - M L_2 + M L_2 - M^2}{L_1 - M} \right) \frac{di_2}{dt} \end{aligned}$$

Equate the last terms in the two lines above

$$L_{eq} \left(\frac{L_1 + L_2 - 2M}{L_1 - M} \right) \frac{di_2}{dt} = \left(\frac{L_1 L_2 - M^2}{L_1 - M} \right) \frac{di_2}{dt}$$

$$\Rightarrow \underline{\underline{L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}}}$$

Q.E.D.

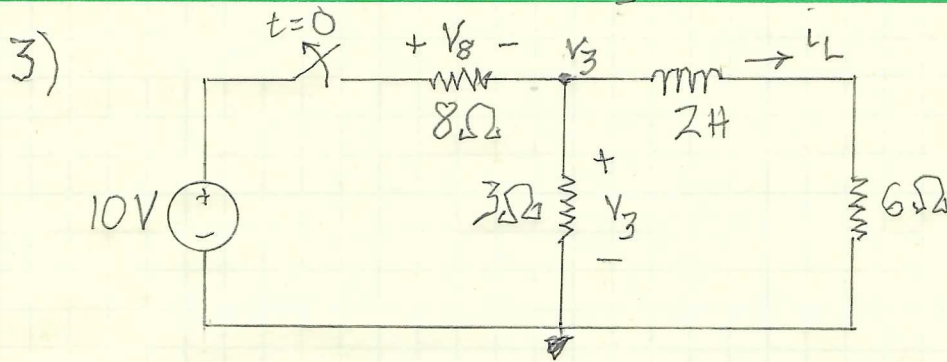

a) For $t=0^-$, inductor is a short, $\Rightarrow 3\Omega \parallel 6\Omega = 2\Omega$
 Voltage division to find $V_3(0^-) = \frac{2}{2+8} 10V = 2V = \underline{\underline{V_3(0^-)}}$
 $i_L(0^-) = \frac{V_3(0^-)}{6\Omega} = \underline{\underline{\frac{1}{3} A = i_L(0^-)}}$

b) $i_L(0^+) = i_L(0^-) = \underline{\underline{\frac{1}{3} A}}$

$V_3(0^+) = -i_L(0^+) 3\Omega = \underline{\underline{-1V}}$

c) With switch open, resistance seen by inductor is $3\Omega + 6\Omega = 9\Omega$,
 $\Rightarrow \tau = L/R_{eq} = \underline{\underline{2H/9\Omega = 222.2ms}}$

d)


$$i_L(t) = \begin{cases} \frac{1}{3} A & t \leq 0 \\ \frac{1}{3} e^{-\frac{9}{2}t} A & t \geq 0 \end{cases} \quad V_3(t) = \begin{cases} 2V & t < 0 \\ -e^{-\frac{9}{2}t} V & t > 0 \end{cases}$$

$V_8(0^-) = \frac{8\Omega}{8\Omega + 2\Omega} 10V = 8V$

$V_8(0^+) = 0V$

$V_8(t) = \begin{cases} 8V & t < 0 \\ 0V & t > 0 \end{cases}$

4)

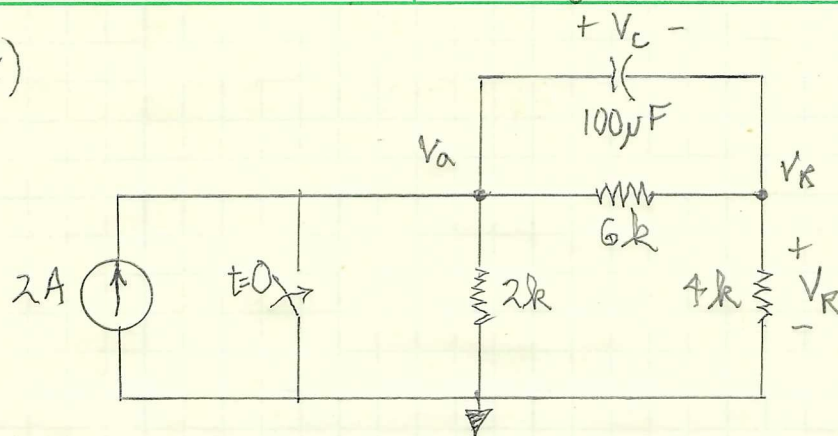

a) For $t=0^-$, capacitor is open circuit. Current source sees resistance of $2k \parallel (4k+6k) = 1667 \Omega$.

$$\Rightarrow V_a(0^-) = (2A)1667 \Omega = 3333V, \quad \Rightarrow V_R(0^-) = \frac{4k}{4k+6k} 3333V = 1333V$$

So, voltage across capacitor is voltage across $6k \Omega$:

$$V_c(0^-) = V_c(0) = V_a(0^-) - V_R(0^-) = 2000V$$

$$\text{Energy stored} = \frac{1}{2} V C^2 = \frac{1}{2} 100 \times 10^{-6} (2000)^2 = \underline{\underline{200 J}}$$

b) Resistance seen by capacitor after the switch is closed is $6k \parallel 4k = 2400 \Omega$ ($2k$ resistor is shorted out.)

$$\Rightarrow RC = (2400)(100 \times 10^{-6}) = \underline{\underline{0.24 s}}$$

c) For $t > 0$, capacitor & $4k$ resistor are in parallel, but their indicated polarities are reversed: $V_c(t) = -V_R(t)$ for $t > 0$.

$$\Rightarrow V_c(t) = \begin{cases} 2000V & t \leq 0 \\ 2000e^{-t/0.24}V & t \geq 0 \end{cases}$$

$$V_R(t) = \begin{cases} 1333V & t < 0 \\ -2000e^{-t/0.24}V & t > 0 \end{cases}$$