

$$1) a) 3\cos(\omega t) + 4\cos(\omega t) \Rightarrow 3\angle 0^\circ + 4\angle 0^\circ = \underline{\underline{7\angle 0^\circ = 7}}$$

$$b) 3\cos(\omega t) + 4\sin(\omega t) \Rightarrow 3 - j4 = \underline{\underline{5\angle -53.13^\circ = 5\angle -0.9273 \text{ rad}}}$$

$$c) 3\cos(\omega t) + 4\sin(\omega t - \pi/2) \Rightarrow 3 - j4e^{j\pi/2} = 3 - j(-j)4 = 3 - 4$$

$$= -1\angle 0^\circ = \underline{\underline{1\angle 180^\circ = 1\angle \pi \text{ rad}}}$$

$$d) 3\cos(\omega t + \pi/3) + 4\sin(\omega t - \pi/3) \Rightarrow 3e^{j\pi/3} - j4e^{-j\pi/3} = 3e^{j\pi/3} + 4e^{-j(\pi/2 + \pi/3)}$$


$$= 3\left(\cos\left(\frac{\pi}{3}\right) + j\sin\left(\frac{\pi}{3}\right)\right) + 4\left(\cos\left(-\frac{5\pi}{6}\right) + j\sin\left(-\frac{5\pi}{6}\right)\right)$$

$$= \frac{3}{2} + j\frac{3\sqrt{3}}{2} - 2\sqrt{3} - j2 = \frac{3-4\sqrt{3}}{2} + j\frac{3\sqrt{3}-4}{2} = \underline{\underline{2.053\angle 163.1^\circ = 2.053\angle 2.84 \text{ rad}}}$$

$$e) 3\cos(\omega t + \pi) + 4\sin(\omega t) = 3e^{j\pi} - j4 = -3 - j4$$


$$= \underline{\underline{5\angle -126.8^\circ = 5\angle -2.214 \text{ rad}}}$$

2)

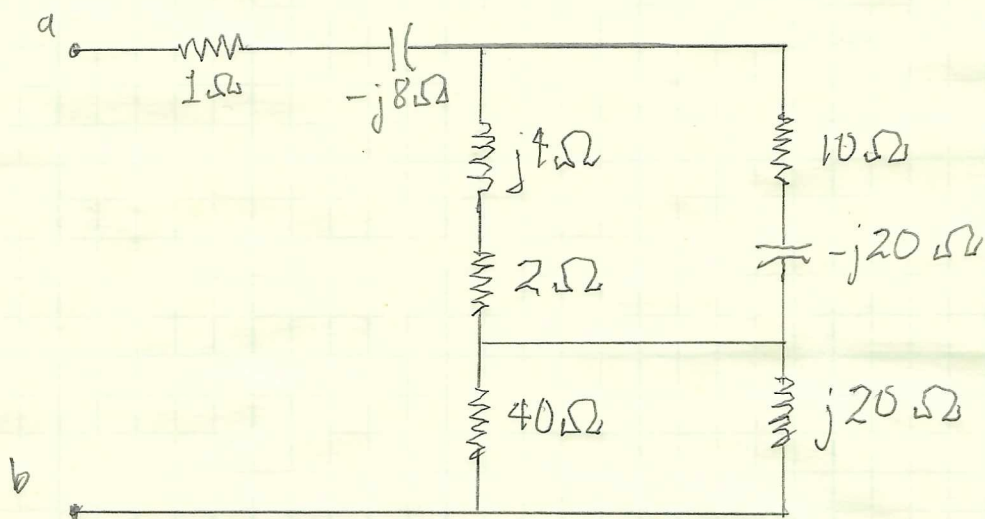

$$\begin{aligned}
 Z_{ab} &= (1 - j8) + (2 + j4) \parallel ((10 - j20) + 40) \parallel j20 \\
 &= (1 - j8) + (3 + j4) + (8 + j16) \\
 &= \underline{\underline{12 + j12 \, \Omega}}
 \end{aligned}$$

3)

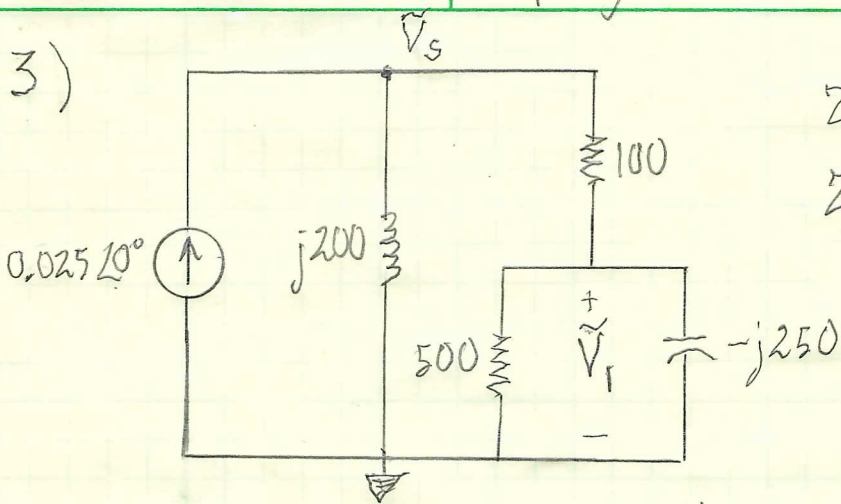

$$Z_L = j50000(0.004) = j200 \Omega$$

$$Z_C = -j \frac{1}{50000 \cdot 80 \times 10^{-9}} = -j250 \Omega$$

Impedance seen by source: $j200 \parallel (100 + 500 \parallel -j250)$

$$= j200 \parallel (100 + 100 - j200) = j200 \parallel (200 - j200) = 200 + j200 \Omega$$

$$\Rightarrow \text{Voltage across source} = (0.025 \text{ A})(200 + j200 \Omega) = 5 + j5 \text{ V} = \tilde{V}_s$$

Can now use voltage division to find $\tilde{V}_1$.


$$500 \parallel -j250 = 100 - j200$$

$$\tilde{V}_1 = \frac{100 - j200}{100 + (100 - j200)} \tilde{V}_s = \frac{100 - j200}{200 - j200} (5 + j5) = 5 + j2.5$$

$$= 5.59 / 26.565^\circ = 5.59 / 0.4636 \text{ rad}$$

$$\Rightarrow \underline{\underline{v_1(t) = 5.59 \cos(50000t + 26.565^\circ) = 5.59 \cos(50000t + 0.4636) \text{ V}}}$$

4)

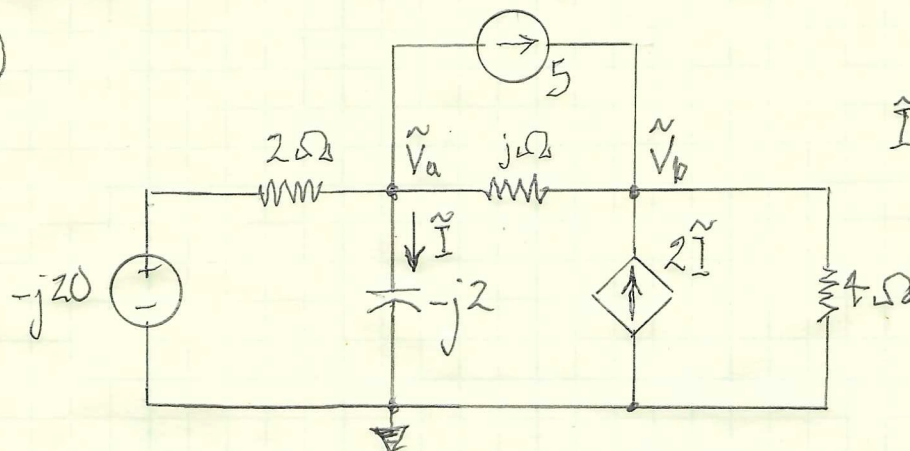

$$\tilde{I} = \frac{\tilde{V}_a}{-j2} = j\frac{1}{2}\tilde{V}_a$$

$$\text{KCL @ } \tilde{V}_a: \frac{\tilde{V}_a + j20}{2} + \frac{\tilde{V}_a}{-j2} + \frac{\tilde{V}_a - \tilde{V}_b}{j} + 5 = 0$$

$$\text{Regroup} \Rightarrow \left(\frac{1}{2} + j\frac{1}{2} - j\right)\tilde{V}_a + j\tilde{V}_b = 5 - j10$$

$$\Rightarrow \left(\frac{1}{2} - j\frac{1}{2}\right)\tilde{V}_a + j\tilde{V}_b = 5 - j10 \quad (1)$$

$$\text{KCL @ } \tilde{V}_b: \frac{\tilde{V}_b - \tilde{V}_a}{j} - 2\tilde{I} + \frac{\tilde{V}_b}{4} - 5 = 0$$

$$\text{Regroup and use } \tilde{I} = j\frac{1}{2}\tilde{V}_a \Rightarrow (j - j)\tilde{V}_a + \left(\frac{1}{4} - j\right)\tilde{V}_b = 5$$

$$\Rightarrow \tilde{V}_b = \frac{5}{\frac{1}{4} - j} = 1.1765 + j4.706 \text{ V}$$

Use this expression for $\tilde{V}_b$ in (1) to obtain $\tilde{V}_a$:

$$\tilde{V}_a = \frac{1}{\left(\frac{1}{2} - j\frac{1}{2}\right)} (5 - j10 - j\tilde{V}_b) = (10.882 - j11.471) \text{ V}$$


$$\tilde{I} = j\frac{1}{2}\tilde{V}_a = 5.7353 + j5.4412 = \underline{\underline{7.9057/43.493^\circ = 7.9057/0.7591 \text{ rad A}}}$$

$$5) f = 50 \text{ kHz} \Rightarrow \omega = 2\pi 50 \times 10^3 \text{ rad/s} = \pi 10^5 \text{ rad/sec}$$

$$L = 4 \mu\text{H} \Rightarrow Z_L = j\omega L = j(\pi 10^5)(4 \times 10^{-6}) = j\pi 0.4 \Omega$$

$$C = 2.4 \mu\text{F} \Rightarrow Z_C = -j\frac{1}{\omega C} = -j\frac{1}{(\pi 10^5)(2.4 \times 10^{-6})} = -j\pi 0.24$$

a)

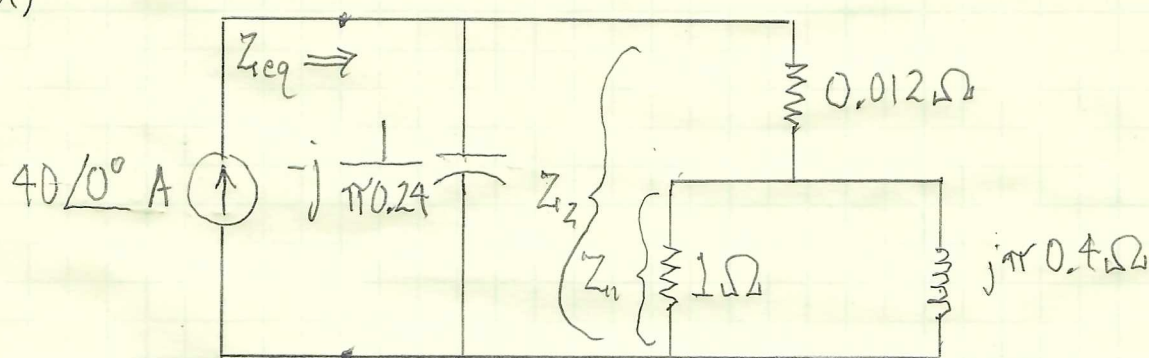

b) To find peak voltage, find Z_{eq} of all elements then multiply by current into that impedance.

$$Z_1 = 1 \Omega \parallel j\pi 0.4 = \frac{j\pi 0.4}{1 + j\pi 0.4} = 0.6123 + j0.4872 \Omega$$

$$Z_2 = 0.012 + Z_1 = 0.6243 + j0.4872 \Omega$$

$$Z_{eq} = -j\frac{1}{\pi 0.24} \parallel Z_2 = 1.0043 \angle 1.3214^\circ$$

$$\text{Voltage across capacitor} = \text{Re} \left[1.0043 \angle 1.3214^\circ \times 40 \angle 0^\circ e^{j\omega t} \right]$$

$$= 40.1712 \cos(\omega t + 1.3214^\circ) \text{ V}$$

$$\Rightarrow \underline{\underline{\text{Peak voltage} = 40.1712 \text{ V}}}$$