

1) a) $R_{eq} = 133 \parallel (65 + 160 \parallel (240 + 400) + 35) \Omega$

b) $R_{eq} = 133 \parallel (100 + 160 \parallel 640) = 133 \parallel (100 + 128) = 133 \parallel 228 = \underline{\underline{84 \Omega}}$

2) a) $V_R = (20 \Omega)(2A) = \underline{\underline{40V}}$, b) $P_V = (2A)(50V) = \underline{\underline{100W}}$

c) Voltage across current source is $50V + V_R = 90V = V_i$.

$\Rightarrow P_i = -(90V)(2A) = \underline{\underline{-180W}}$

d) stay the same because $P_V = (2A)(50V)$ independent of R .

e) Decrease because $P_i = -(50 + 2R)(2A)$.

3) a) True $V_1 = V_2 + V_3 \Rightarrow V_1 > V_2$

b) False $\bar{i}_2 = \bar{i}_3$

c) False $R_1 < R_2 + R_3$ so more current goes through R_1 .

d) False $V_2 = \bar{i}_2 R_2 = \bar{i}_3 R_2 < \bar{i}_3 R_3 = V_3$.

e) False $P_i = -(1A)^2 (R_1 \parallel R_2)$

f) True No current through R_2 or $R_3 \Rightarrow P_i = -(1A)^2 R_1$

4) a) $-V_S + V_1 + V_2 = 0 \Rightarrow \underline{\underline{V_S = \bar{i}_1 R_1 + \bar{i}_2 R_2}}$

b) $\underline{\underline{\bar{i}_1 + \bar{i}_S = \bar{i}_2}}$

c) $V_a = V_2 = \underline{\underline{\bar{i}_2 R_2 = V_a}}$

d) $V_1 = V_S - V_a = \bar{i}_1 R_1 \Rightarrow \underline{\underline{V_a = V_S - \bar{i}_1 R_1}}$

5) a) $V_\Delta = \frac{5}{10+5} (45V) = \underline{\underline{15V}}$

b) $0.2 V_\Delta = 3A$, $R_{eq} = 12 \parallel 60 = 10 \Omega$, $\bar{i}_2 = \frac{10 \Omega}{60 \Omega} 3A = \underline{\underline{0.5A}}$

c) $V_a = (3A) R_{eq} = (3A)(10 \Omega) = \underline{\underline{30V}}$

d) $R_{eq} = 90 \parallel (10+5) = \frac{90 \cdot 15}{90+15} = \frac{18 \cdot 15}{18+3} = \frac{270}{21} = 12.857 \Omega$

$P = -\frac{V^2}{R_{eq}} = -\frac{(45)^2}{(270/21)} = \underline{\underline{-157.5W}}$