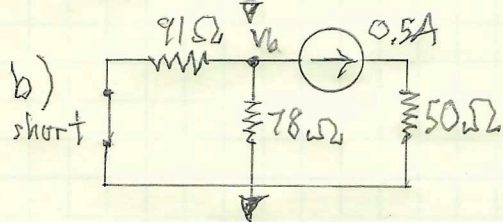


Voltage division:  $V_a = \frac{78\Omega}{78\Omega + 91\Omega} 39V = \underline{\underline{18V}}$



$$91\Omega \parallel 78\Omega = 42\Omega$$

$$V_b = -(0.5A)(42\Omega) = \underline{\underline{-21V}}$$

c)  $V_c = V_a + V_b = \underline{\underline{-3V}}$  To check, could use nodal analysis.

$$\Rightarrow \frac{V_c - 39}{91} + \frac{V_c}{78} + 0.5 = 0 \Rightarrow \left(\frac{1}{91} + \frac{1}{78}\right)V_c = -0.5 + \frac{39}{91} \Rightarrow V_c = -3V$$

2) a) Deactivate source,  $105\Omega$  shorted out.  $\Rightarrow R_N = \underline{\underline{70\Omega}}$

b) With short across a & b,  $I_{sc} = I_N = 1A + \frac{35V}{70\Omega} = \underline{\underline{1.5A}}$

c)  $R_L = R_N = 70\Omega$ . Power =  $I^2 R_L = \left(\frac{1.5A}{2}\right)^2 70\Omega = \underline{\underline{39.375W}}$

3) a)  $V_\Delta = R_2 \bar{i}_2$

b)  $\bar{i}_1 + \alpha V_\Delta = \bar{i}_2 \Rightarrow \bar{i}_1 + \alpha R_2 \bar{i}_2 = \bar{i}_2 \Rightarrow \underline{\underline{\bar{i}_1 + (\alpha R_2 - 1)\bar{i}_2 = 0}}$

c)  $\bar{i}_1 R_1 + \bar{i}_2 R_2 + V_S = 0$

d)  $\underline{\underline{V_a = -\bar{i}_1 R_1}}$

e)  $\underline{\underline{V_a = \bar{i}_2 R_2 + V_S}}$

4) a)  $\bar{i}_\Delta = \frac{V_a}{45\Omega}$

b)  $\bar{i}_1 = \frac{V_a + 9\bar{i}_\Delta - 84V}{12\Omega} = \frac{V_a + 9\left(\frac{V_a}{45}\right) - 84}{12} = \underline{\underline{\left(\frac{1}{12} + \frac{1}{60}\right)V_a - 7}}$

c)  $\left(\frac{1}{12} + \frac{1}{60}\right)V_a - 7 + \frac{V_a}{45} + \frac{V_a}{90} - 5 = 0$

d)  $\left(\frac{1}{12} + \frac{1}{60} + \frac{1}{45} + \frac{1}{90}\right)V_a = 12 \Rightarrow \underline{\underline{V_a = 90V}}$

5) a)  $V_p = \underline{\underline{0.2V}}$  (by inspection), b)  $V_n = V_p = \underline{\underline{0.2V}}$

c)  $\frac{V_n - (-0.2V)}{10k} + \frac{V_n - V_o}{50k} = 0 = \underline{\underline{\frac{0.2 + 0.2}{10k} + \frac{0.2 - V_o}{50k}}}$

d)  $V_o = 5(0.2 + 0.2) + 0.2 = \underline{\underline{2.2V}}$