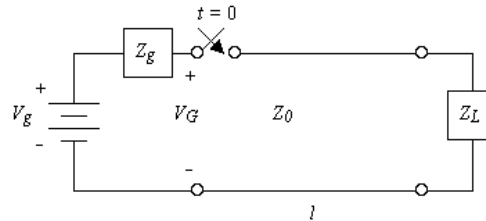


EE331—EXAMPLE #11: BOUNCE DIAGRAM

At $t = 0$ we flip the switch on a circuit with a real load of $150\ \Omega$ attached to a $50\text{-}\Omega$ transmission line 300 m long. If our generator is a DC source of 10 V with a resistance of $30\ \Omega$, and the wave velocity is $3 \times 10^8\text{ m/s}$, (a) use a bounce diagram to sketch the voltage at the load as a function of time for $0 \leq t \leq 10\ \mu\text{s}$. (b) Find the steady-state voltage.

(a) First make a sketch of the transmission line and identify the quantities.




Find the period T , the reflections coefficients Γ_L and Γ_G , and V_1^+ :

$$T = \frac{l}{u} = \frac{300}{3 \times 10^8} = 10^{-6}\text{ s} = 1\ \mu\text{s}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{150 - 50}{150 + 50} = \frac{1}{2}$$

$$\Gamma_G = \frac{Z_g - Z_0}{Z_g + Z_0} = \frac{30 - 50}{30 + 50} = -\frac{1}{4}$$
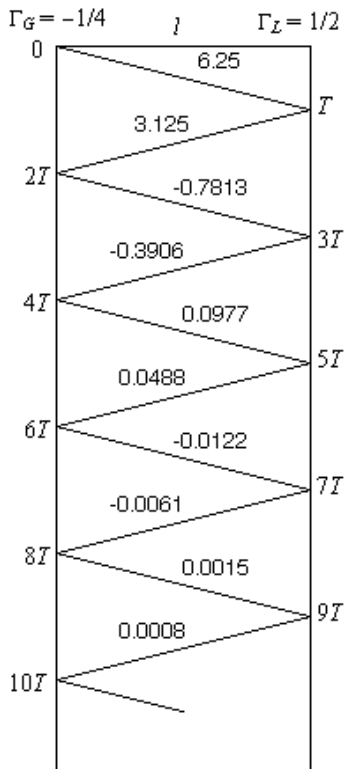
$$V_1^+ = \frac{Z_0}{Z_g + Z_0} V_g = \left(\frac{50}{30 + 50} \right) 10 = 6.25\text{ V}$$



$$0 \leq t < T: V_L = 0$$

$$T \leq t < 3T: V_L = V_1^+ + V_1^-$$

$$= 6.25 + 3.125 = 9.375\text{ V}$$

$$3T \leq t < 5T: V_L = 9.375 + V_2^+ + V_2^-$$

$$= 9.375 - 0.7813 - 0.3906 = 8.2031\text{ V}$$

$$5T \leq t < 7T: V_L = 8.2031 + V_3^+ + V_3^-$$

$$= 8.2031 + 0.0977 + 0.0488 = 8.3496\text{ V}$$


$$7T \leq t < 9T: V_L = 8.3496 + V_4^+ + V_4^-$$

$$= 8.3496 - 0.0122 - 0.0061 = 8.3313\text{ V}$$

$$9T \leq t < 11T: V_L = 8.3313 + V_5^+ + V_5^-$$

$$= 8.3313 + 0.0015 + 0.0008 = 8.3336\text{ V}$$

Now sketch $V_L(t)$:

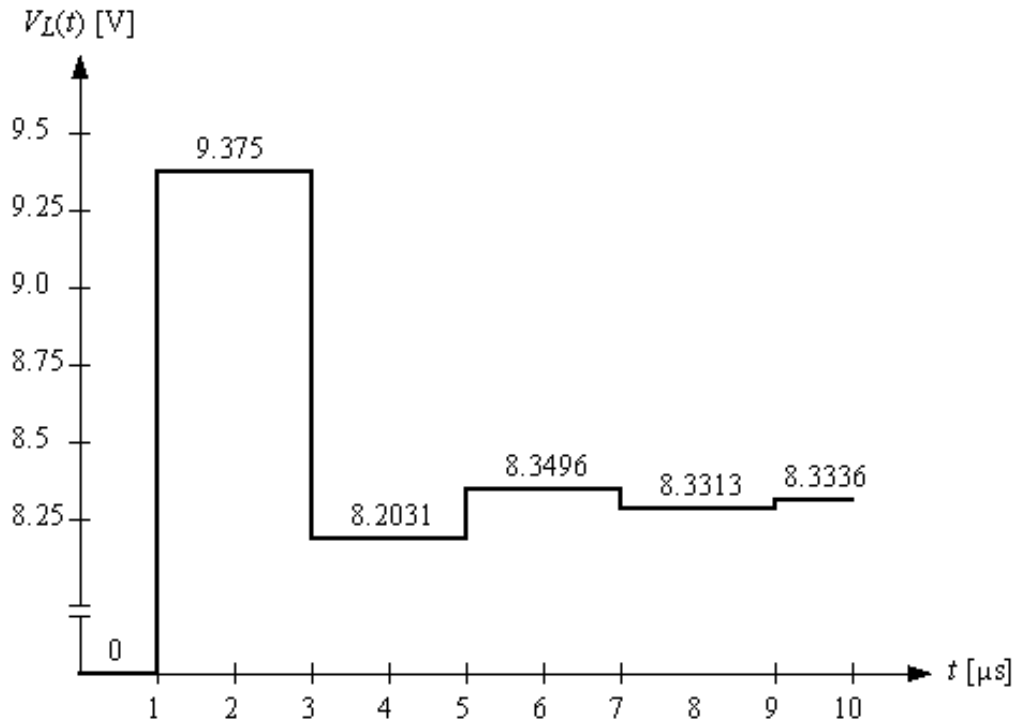

(b) At steady state:

$$V_L = V_\infty = \frac{Z_L}{Z_g + Z_L} V_g = \left(\frac{150}{30 + 150} \right) 10 = 8.3333 \text{ V}$$