

The input impedance of a line  $Z_{in}$  can be generalized to be the “input” impedance of a line looking toward the load measured anywhere along the line.

$$Z'_{in} = \frac{V_s(z)}{I_s(z)} = Z_0 \left( \frac{Z_L - Z_0 \tanh(\gamma z)}{Z_0 - Z_L \tanh(\gamma z)} \right) \quad (1)$$

where  $z$  is a negative value (since the load is at  $z = 0$ ). For a lossless line this becomes:

$$Z'_{in} = \frac{V_s(z)}{I_s(z)} = Z_0 \left( \frac{Z_L - jZ_0 \tan(\beta z)}{Z_0 - jZ_L \tan(\beta z)} \right) \quad (2)$$

(Why?) For a lossless line of length  $l$  m, the input impedance at the generator is:

$$Z_{in} = \frac{V_s(-l)}{I_s(-l)} = Z_0 \left( \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right) \quad (3)$$

(a) Why is there a sign change between Eqs. (2) and (3)? (b) Something magical happens to the input impedance when  $l$  is a multiple of  $\lambda/2$ —i.e., a multiple of half a wavelength. What does it become?

(a) There's a sign change because  $\tan(\beta z)$  is an odd function:

$$\tan(\beta z) = \frac{\sin(\beta z)}{\cos(\beta z)} = \frac{\sin(-\beta l)}{\cos(-\beta l)} = \frac{-\sin(\beta l)}{\cos(\beta l)} = -\tan(\beta l)$$

(b) For  $l = \frac{n\lambda}{2}$ ,  $n = 1, 2, 3, \dots$

$$\beta l = \frac{2\pi}{\lambda} \cdot \frac{n\lambda}{2} = n\pi$$

and so

$$\tan(\beta l) = \tan(n\pi) = \frac{\sin(n\pi)}{\cos(n\pi)} = 0$$

Thus,

$$Z_{in} = Z_0 \left( \frac{Z_L + 0}{Z_0 + 0} \right)$$

or

$$Z_{in} = Z_L$$

for  $l = \text{multiples of } \lambda/2$ ! In words, when the length of a transmission line is a multiple of half a wavelength, the input impedance is equal to the load impedance. Cool, eh?