

EE331—EXAMPLE #7: TL AVERAGE POWER TO THE LOAD

A transmission line with a characteristic impedance of $50\ \Omega$ is connected to a load with an impedance of $100\ \Omega$. What fraction of power is delivered to this load relative to the power delivered if the load were matched?

The average power delivered to the load is given by:

$$P_{L_{ave}} = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} (1 - |\Gamma_L|^2) \quad [\text{W}]$$

For a perfectly-matched load, $|\Gamma_L| = 0$ (i.e., there's no reflection). Thus,

$$P_{L_{max}} = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \quad [\text{W}]$$

For our problem, $Z_0 = 50\ \Omega$ and $Z_L = 100\ \Omega$. Therefore, Γ_L is:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 - 50}{100 + 50} = \frac{50}{150} = \frac{1}{3}$$

and

$$|\Gamma_L| = \frac{1}{3}$$

The fraction of power is given by $P_{L_{ave}}/P_{L_{max}}$:

$$P_{L_{ave}}/P_{L_{max}} = \frac{\frac{1}{2} \frac{|V_0^+|^2}{Z_0} (1 - \frac{1}{3}^2)}{\frac{1}{2} \frac{|V_0^+|^2}{Z_0}} = 1 - \frac{1}{9} = \frac{8}{9}$$