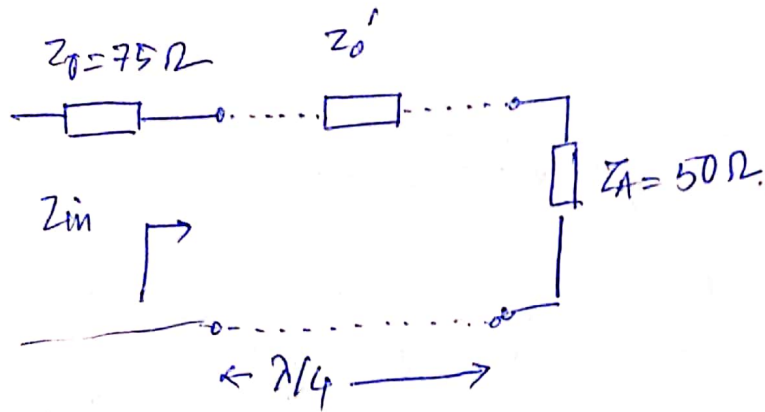


1.



Let, the characteristic impedance of the transmission line connecting the 75Ω transmission line and the antenna (of impedance $Z_A = 50 \Omega$) be Z_0' . The length of this line is $l = \lambda/4$. $\rightarrow$ Quarter-wave length transformer.

The purpose of the quarter-wave length transformer is to match the antenna load with that of the transmission line of ($Z_0 = 75 \Omega$).

Hence, the input impedance as seen by the transmission line should also be ($Z_{in} = 75 \Omega$)

$$Z_{in}(l = \lambda/4) = Z_0' \left(\frac{Z_A + jZ_0 \tan(\beta l)}{Z_0 + jZ_A \tan(\beta l)} \right) \Bigg|_{l = \lambda/4}$$

The diagram shows a transmission line with characteristic impedance Z_0' connected to a load Z_A . The input impedance is Z_{in} .

$$\beta l \Big|_{l = \lambda/4} = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2}$$

$$\tan\left(\frac{\pi}{2}\right) \rightarrow \infty$$

$$\therefore Z_{in}(l = \lambda/4) = Z_0' \frac{Z_A + jZ_0 \tan(\beta l)}{Z_0 + jZ_A \tan(\beta l)} \Bigg|_{\tan(\beta l) \rightarrow \infty}$$

$$= \frac{(Z_0')^2}{Z_A}$$


$$Z_{in} = \frac{Z_0'^2}{Z_A}$$

$$\Rightarrow Z_0' = \sqrt{Z_{in} Z_A} = \sqrt{75 \times 50} = 61.23 \Omega \text{ (Ans)}$$

$$\text{Length of the line} = \frac{\lambda}{4} = \frac{u}{4f} = \frac{3 \times 10^8}{4 \times (97.1 \times 10^6)} = 0.772 \text{ m} \\ = 77.2 \text{ cm (Ans).}$$

b) Power delivered to the antenna is expressed as $\rightarrow$ without matched line

$$P_{av} = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} [1 - |\Gamma|^2]$$

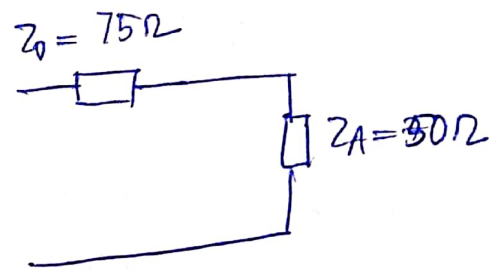

$$\Gamma = \frac{Z_A - Z_0}{Z_A + Z_0} = \frac{50 - 75}{50 + 75} \\ = \frac{-25}{125} = -\frac{1}{5}$$

$$P_{av} = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \left\{ 1 - \left(\frac{1}{5}\right)^2 \right\}$$

Power delivered to the antenna with matched line ($\Gamma=0$)

$$\therefore P_{av}' = \frac{1}{2} \frac{|V_0^+|^2}{Z_0}$$

$$\therefore \frac{P_{av}}{P_{av}'} = \frac{\left\{ \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \right\} \cdot \frac{1 - \frac{1}{25}}{1}}{\left\{ \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \right\}} = \frac{24}{25} \text{ (Ans)}$$

2) Z_0 (Characteristic impedance) = 50Ω .

Z_L (load impedance) = $(40 - j25) \Omega$.

Z_L (normalized) = $\frac{40 - j25}{50} = 0.8 - j0.5$.

Z_L is given by the point P.


$|\Gamma_L| = \frac{OP}{OQ} = 0.282$ } From Smith's chart.

$\angle \Gamma_L = -96^\circ$.

a) $\Gamma_L = 0.282 \angle -96^\circ$

b) Put the distance of 'OP' on SWR line below, you will get

c) $SWR(s) = 1.8$.

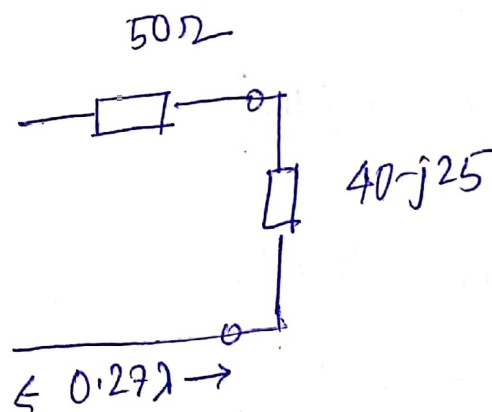

To find Z_{in} , draw the constant VSWR circle with OP as the radius and rotate the point P (in the direction of generator i.e. clockwise by an additional 0.27λ).

Current position of OP $\Rightarrow 0.382\lambda$.

$\therefore$ Position of $Z_{in} \Rightarrow 0.382\lambda + 0.27\lambda = 0.652\lambda$.
 $= (0.652\lambda - 0.5\lambda) = 0.152\lambda$ (in the upper half of chart)

NAME Problem 2

TITLE


DWG. NO.

DATE

SMITH CHART ENGS 120

COLOR BY J. COLVIN, UNIVERSITY OF FLORIDA, 1997

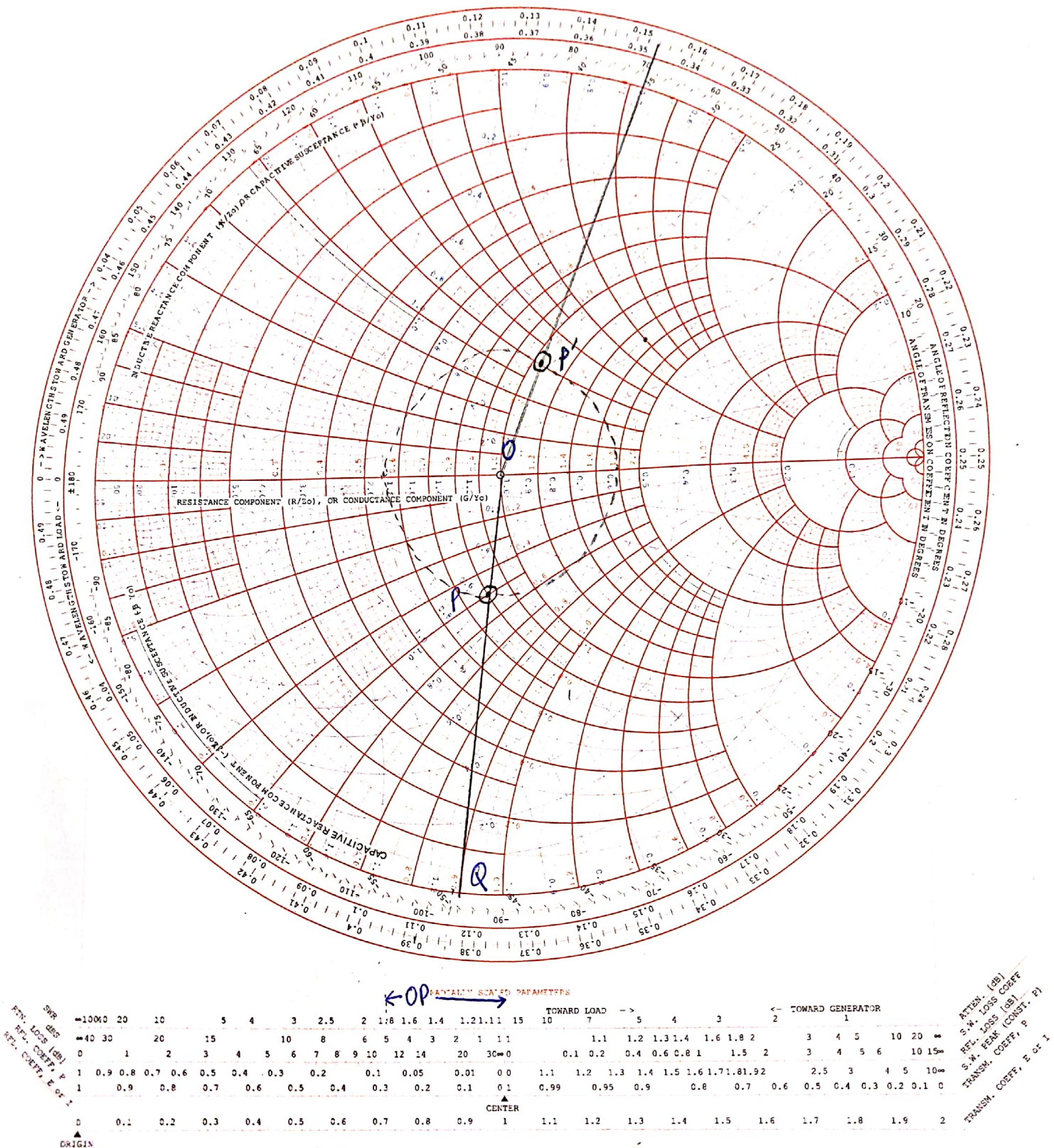NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



The point (Z_{in}) is given by P' .


Page-4

$$Z_{in} \approx (1 + j0.6)$$

$$= (1 + j0.6) \times 50 = (50 + j30) \Omega$$

3) Prob 11.43

a)

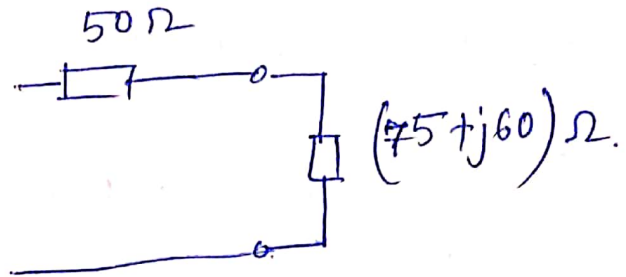

$$Z_L = \frac{75 + j60}{50} = (1.5 + j1.2) \Omega$$

$$\left[\begin{array}{l} |\Gamma_L| = \frac{OP}{OQ} = 0.487 \\ \angle \Gamma_L = 41^\circ = \angle A O Q \end{array} \right] \text{ From Smith chart.}$$

$$\Gamma_L = 0.487 \angle 41^\circ$$

b) SWR is shown below.

$$S = 2.75$$

c) Draw the constant VSWR circle with OP as radius, and rotate 0.2λ towards generator.

Z_{in} is shown by P' .

$$Z_{in} = (0.53 - j0.65) 50 = (26.5 - j32.5) \Omega$$


Problem 3

COLOR BY J. COLVIN, UNIVERSITY OF FLORIDA, 1997

DATE _____

SMITH CHART ENGS 120

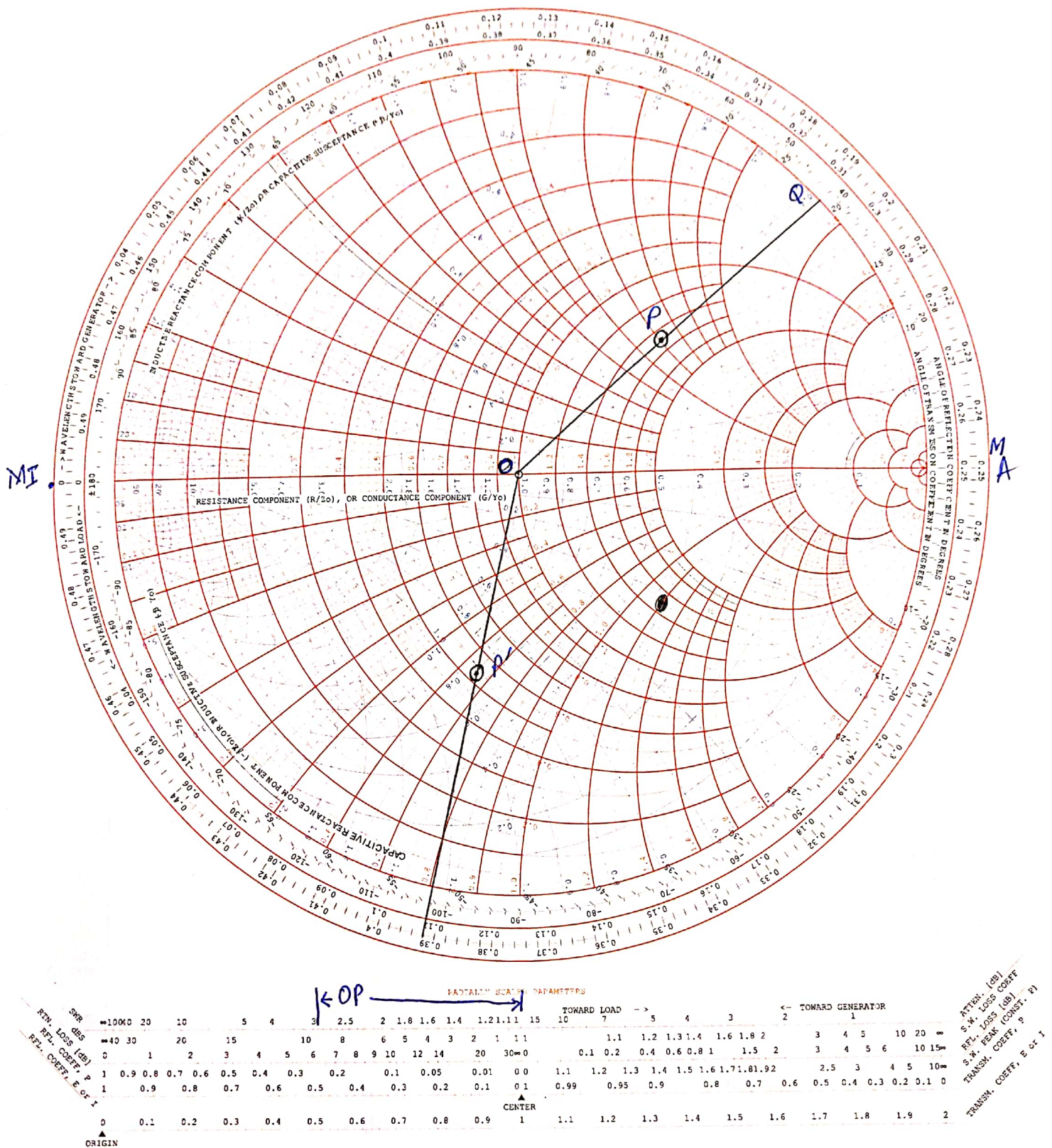NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



d) Minimum voltage occurs when the load is shorted ($r=jx=0$).
 The point of minimum voltage is shown by the extreme ^{left} ~~right~~ point in the chart (MI).


The distance from OQ to MI going towards generator
 $= (0.5\lambda - 0.192\lambda) = 0.308\lambda$.

e) Maximum voltage occurs when the load is opened ($r=jx \rightarrow \infty$).
 The point of maximum voltage is shown by the extreme right point in the chart (MA).

The distance from OQ to MA going towards generator
 $= (0.25\lambda - 0.192\lambda) = 0.058\lambda$.

4) Prob 11.50

a) $s = 2.6$.

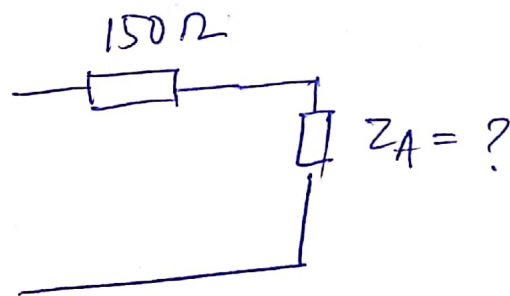

The voltage ^{maxima} and minima are located $\lambda/2$ distance apart.

$$\therefore \lambda/2 = 120 \text{ cm} \Rightarrow \lambda = 240 \text{ cm}.$$

$$f = \frac{u}{\lambda} = \frac{3 \times 10^8}{2.4} = 125 \text{ MHz}$$

b). The last maximum is 40 cm from the antenna

$$40 \text{ cm} = \frac{40}{240} \lambda = 0.167 \lambda.$$

Draw the constant VSWR ($S=2.6$) circle and the antenna is located at 0.167λ 'towards load' from the maximum voltage (extreme right) point given by M_A

$$\begin{aligned} \text{location of antenna} &= (0.25 \lambda + 0.167 \lambda) \\ &= 0.417 \lambda \quad (\text{upper half plane of the Smith's chart}) \end{aligned}$$

location of antenna $\rightarrow OP$.

$$Z_A = (0.48 + \cancel{0.002} j 0.48)$$

$$= (0.48 + j 0.48) 150$$

$$= (72 + j 72) \Omega. \quad (\text{Ans}).$$