

EE331 — Homework #5 / Due Friday, Feb. 19, 2020 at the beginning of class

Note that you need to show your work on a Smith chart for the Smith chart problems (1 and 2), and you need to turn the charts in as part of your homework. A Smith chart is available on our homework web page.

1. Redo Example #10 but with an antenna impedance of $Z_L = 50 - j25 \Omega$.
2. A shunt stub tuner of length $l = 0.12\lambda$ is used to match a $60\text{-}\Omega$ lossless line to a load. If the stub is located at $d = 0.3\lambda$ from the load, calculate the load *impedance* Z_L . Note the italics!
3. (a) Redo part (a) of Example #11 but rather than finding the voltage at the load, find and sketch the voltage at the midpoint of the line V_M . You can use the bounce diagram from the example. (b) Using the same TL circuit of Example #11, let the DC source be -10 V (everything else is the same) and flip the switch at $t = 1\text{ }\mu\text{s}$. Use a bounce diagram to sketch the voltage at the load as a function of time for $0 \leq t \leq 10\text{ }\mu\text{s}$. (c) Combine (i.e., add) the results from part (a) of Example #11 and part (b) of this problem to find the transient behavior of a $1\text{-}\mu\text{s}$ pulse.