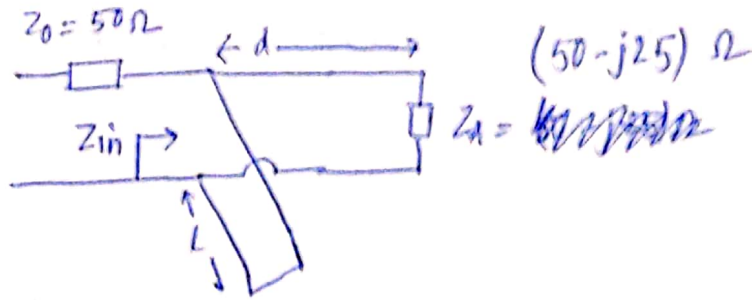


1a)



The shunt short-circuited stub is used to match the ^{antenna} load impedance with that of the transmission line. Hence, the required Z_{in} should be $Z_0 = 50 \Omega$. We have the shunted stub and length (d) from the load to transform the antenna to an equivalent impedance of $Z_{in} = 50 \Omega$.


$$Z_A = \frac{50 - j25}{50} = 1 - j0.5.$$

A straight line passing through center (0) and such that $OY_A = OZ_A$ gives the antenna admittance of $Y_A = 0.8 + j0.4$.

We know, the input impedance (Z_{in}) or input (Y_{in}) has input conductance of ($G_{in} = 1$). Hence, draw ($G=1$) circle on Smith's chart.

The points where the circle ~~off~~ with radius OZ_A for load and ($G=1$) circle meet provide two possible solutions for length of the transmission line (d).

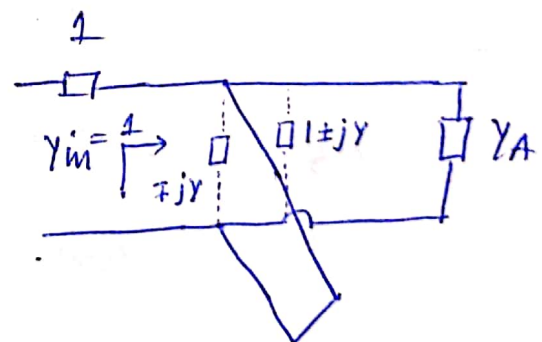As can be seen, Y_A can now be transferred to either point A or B so as to give an admittance of $(Y_A' = 1 \pm jy)$




Length of transmission line to reach A (d_1) = 0.039λ .

Length of transmission line to reach B (d_2) = 0.25λ .

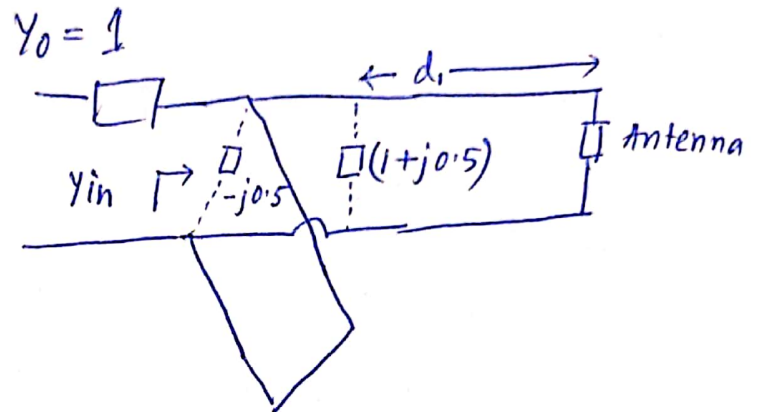b) For point A

$$Y_{A'} = 1 + j0.5$$

Hence, we need a stub of input admittance of $(-j0.5)$ to match the antenna with line



$$Y_{A'} + Y_{stub_1} = Y_0$$

$$Y_{stub_1} = Y_0 - Y_{A'}$$

$$= 1 - (1 + j0.5) = -j0.5$$

Place Y_{stub_1} in Smith' chart and find the length of the stub from the right extreme point.


$$\text{Length of stub } (Y_{stub_1}) \Rightarrow l_1 = 0.176\lambda$$

For point B

$$Y_{A'} = 1 - j0.5$$

$$Y_{A'} + Y_{stub_2} = Y_0$$

$$Y_{stub_2} = 1 - (1 - j0.5) = j0.5$$

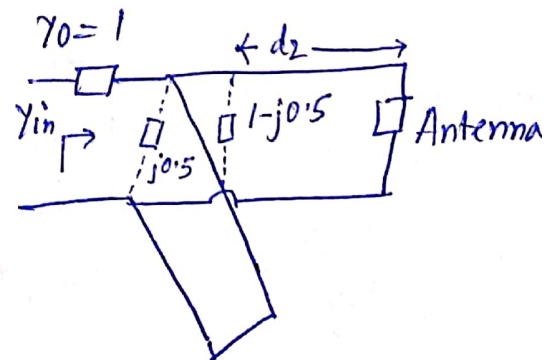

$$\text{Length of } (Y_{stub_2}) \Rightarrow l_2 = 0.324\lambda$$

NAME

Problem 1

TITLE


DWG NO.

SMITH CHART ENCS 120

COLOR BY J. COLVIN UNIVERSITY OF FLORIDA, 1997


DATE

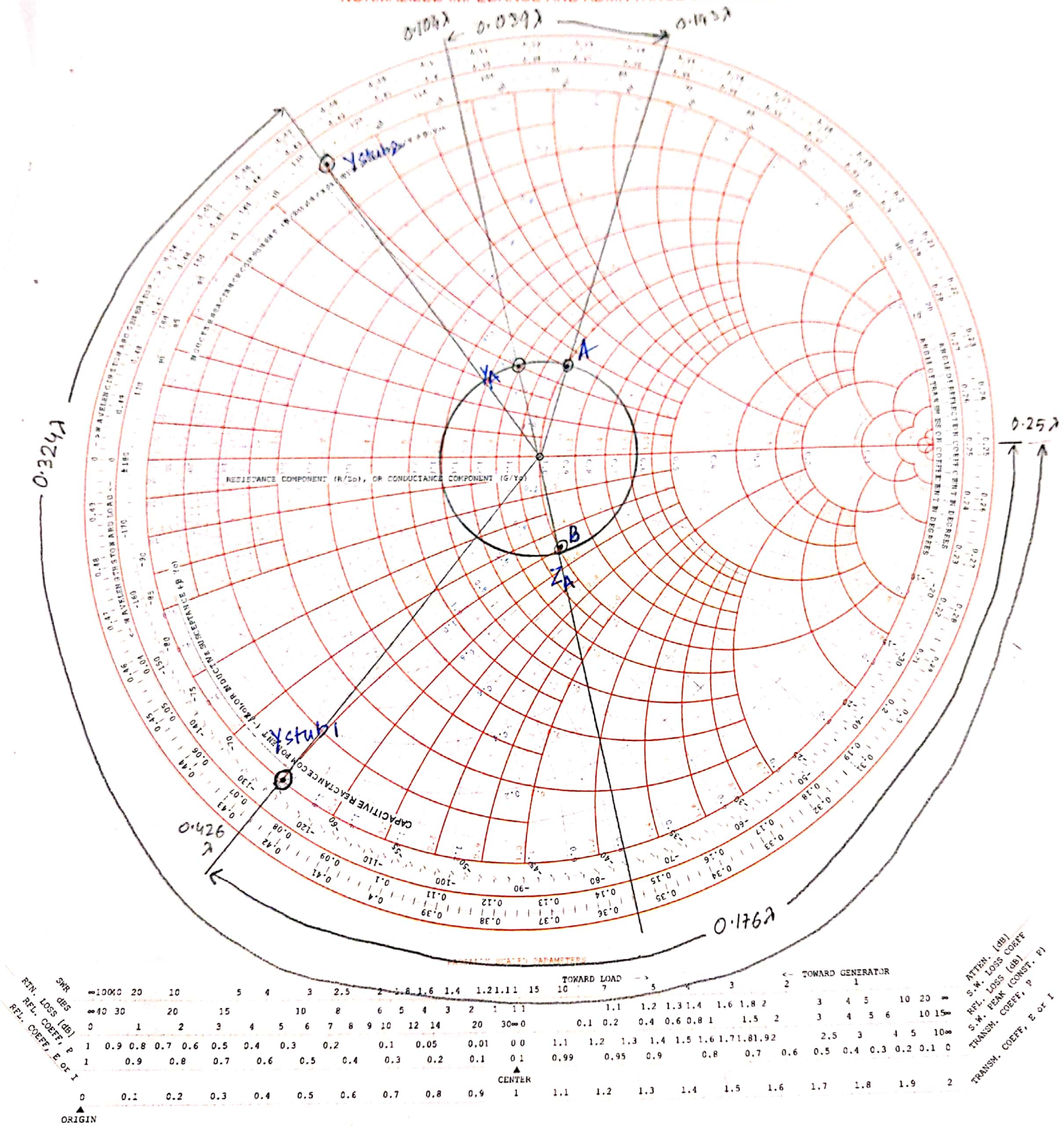NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



2.)

Page-3

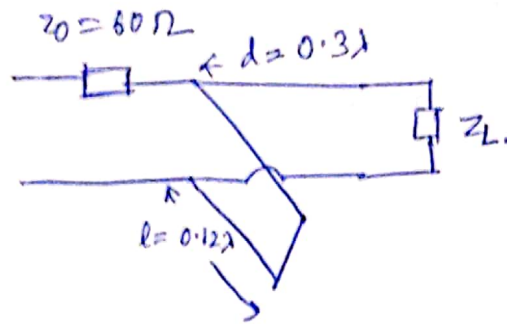


$$Y_{stub}' = -j1.07$$

Hence,

$$Y_{stub}' + Y_L' = Y_0$$

$$Y_L' = Y_0 - Y_{stub}'$$

$$= 1 + j1.07.$$

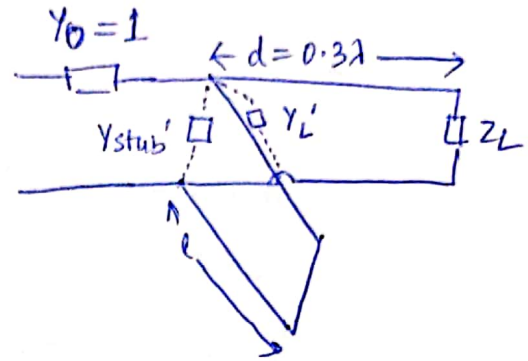

Y_L' is shown in Smith chart. Now, rotate Y_L' towards load by 0.3λ .

The load admittance is Y_L (shown in Smith's chart)

$$Z_L = 0.58 + j0.7$$

$$= (0.58 + j0.7) \times 60 = (34.8 + j42) \Omega.$$


3.)

$$T = \frac{l}{u} = \frac{300}{3 \times 10^8} = 10^{-6} s = 1 \mu s.$$


$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{150 - 50}{150 + 50} = \frac{1}{2}$$

$$\Gamma_G = \frac{Z_g - Z_0}{Z_g + Z_0} = \frac{30 - 50}{150 + 50} = -\frac{1}{4}$$
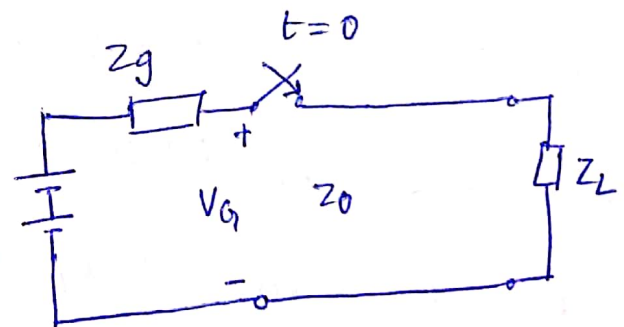
$$V_1^+ = \frac{Z_0}{Z_g + Z_0} V_g = \left(\frac{50}{30 + 50} \right) 10 = 6.25 V$$



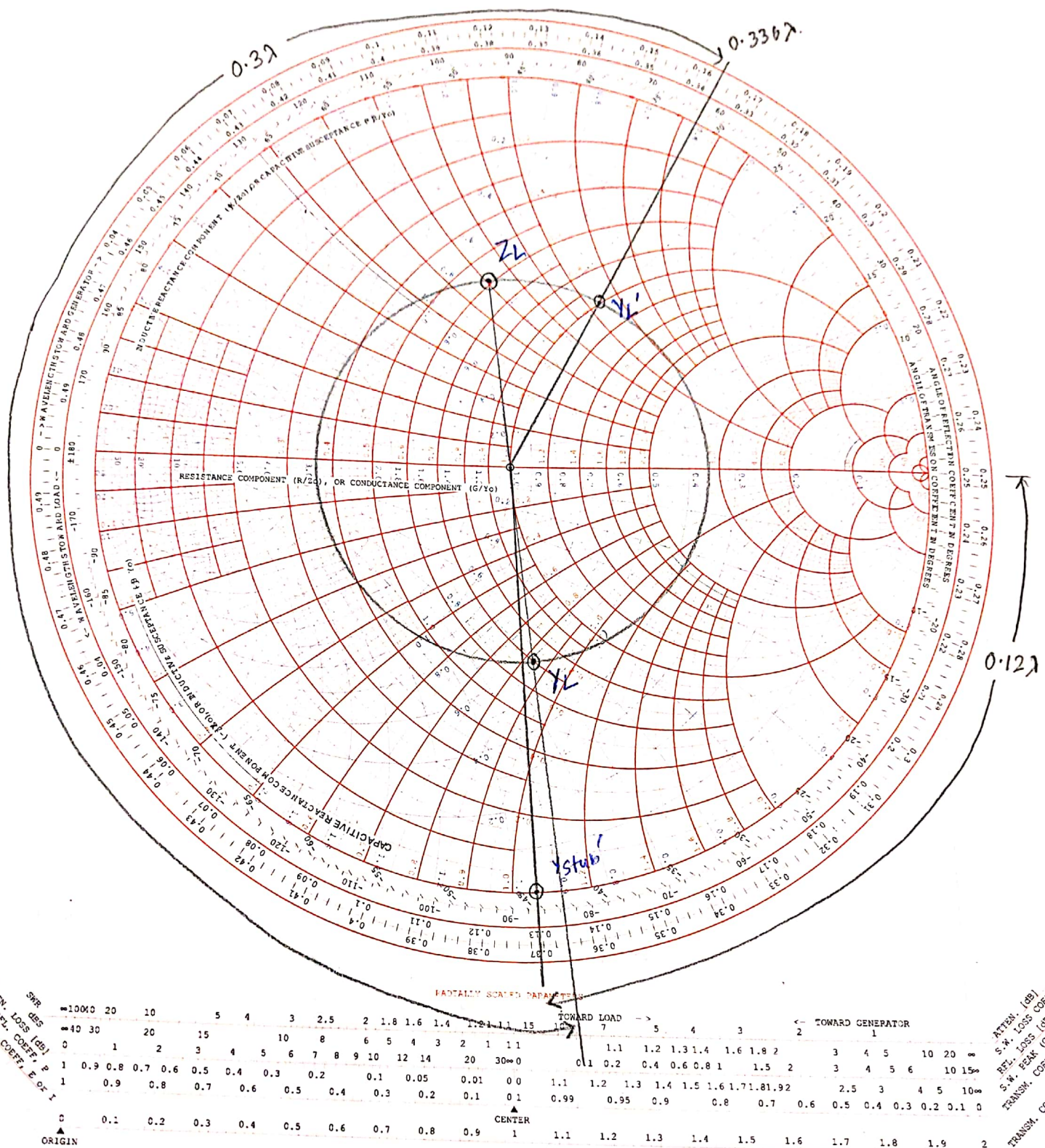NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



Reflex Bounce Diagram

$$V_1^- = \Gamma_L \cdot V_1^+ = \frac{1}{2} \times 6.25 = 3.125 \text{ V.}$$

$$0 \leq t < T/2, V_M = 0$$

$$T/2 \leq t < 3T/2, V_M = 6.25 \text{ V}$$

$$3T/2 \leq t < 5T/2, V_M = 6.25 + 3.125 = 9.375 \text{ V}$$

$$5T/2 \leq t < 7T/2, V_M = 9.375 - 0.7813 = 8.5937 \text{ V}$$

$$7T/2 \leq t < 9T/2, V_M = 8.5937 - 0.3906 = 8.2031 \text{ V.}$$

$$9T/2 \leq t < 11T/2, V_M = 8.2031 + 0.0977 = 8.3008 \text{ V.}$$


$$11T/2 \leq t < 13T/2, V_M = 8.3008 + 0.0488 = 8.3496 \text{ V.}$$


$$13T/2 \leq t < 15T/2, V_M = 8.3496 - 0.0122 = 8.3374 \text{ V.}$$

$$15T/2 \leq t < 17T/2, V_M = 8.3374 - 0.0061 = 8.3313 \text{ V}$$


$$17T/2 \leq t < 19T/2, V_M = 8.3313 + 0.0015 = 8.3328 \text{ V}$$
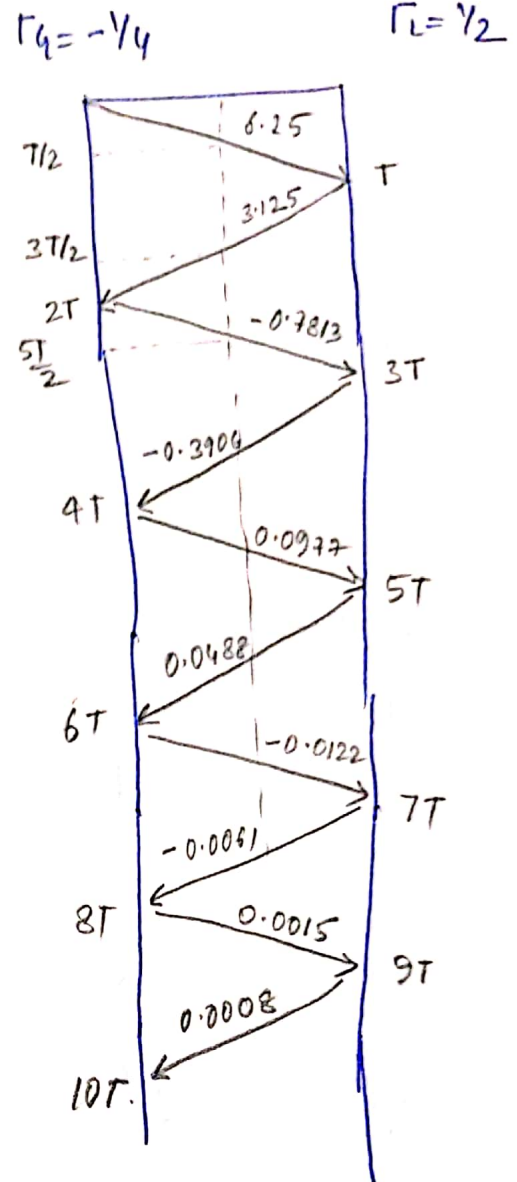
$$19T/2 \leq t < 21T/2, V_M = 8.3328 + 0.0008 = 8.3336 \text{ V}$$



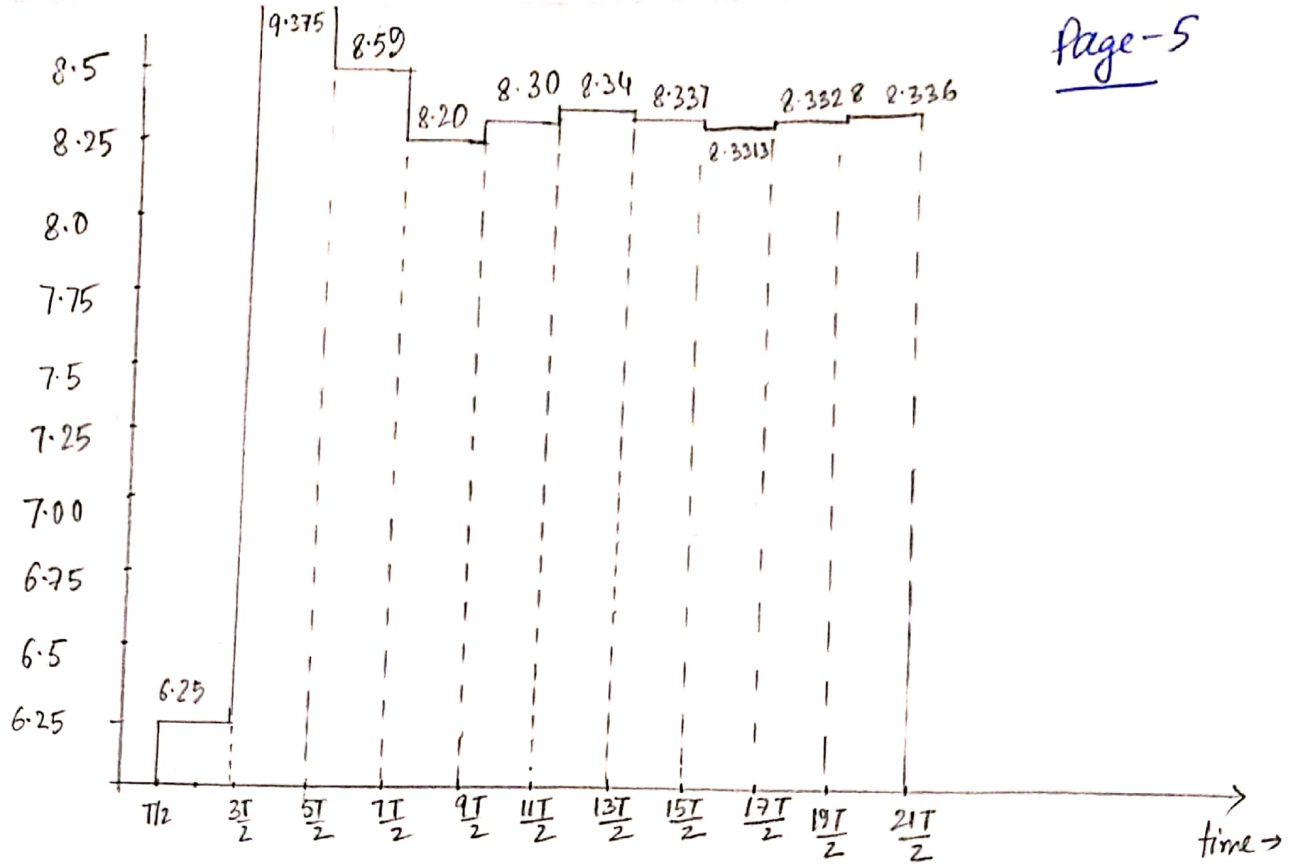

$$T = 1 \mu s.$$

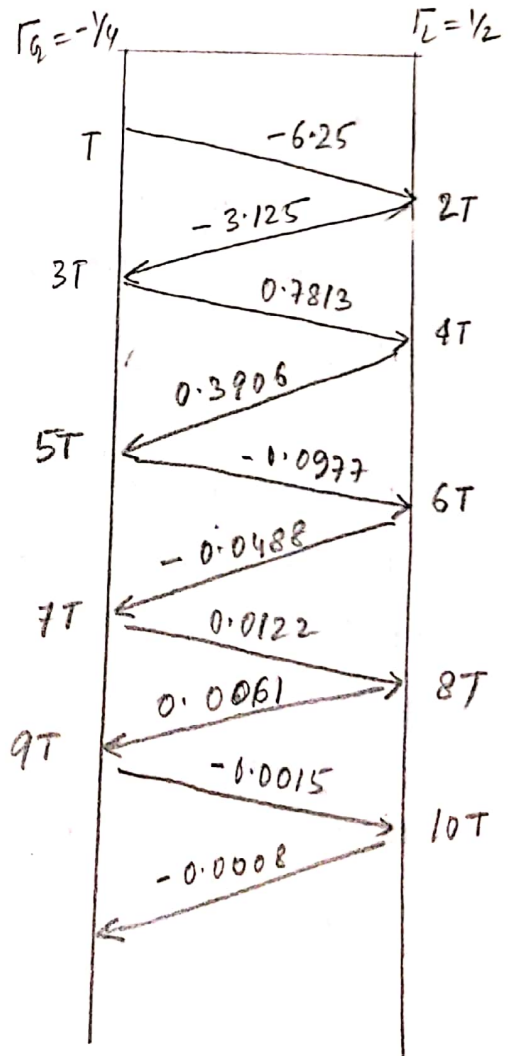

36) $V_g = -10V.$

$$0 \leq t < 2T, V_L = 0$$


$$2T \leq t < 4T, V_L = -6.25 - 3.125 = -9.375 V.$$

$$4T \leq t < 6T, V_L = -9.375 + 0.7813 + 0.3906 = -8.2031 V.$$

$$6T \leq t < 8T, V_L = -8.2031 - 0.0977 - 0.0488 = -8.3492 V$$

$$8T \leq t < 10T, V_L = -8.3492 + 0.0122 + 0.0061 = -8.3312 V$$
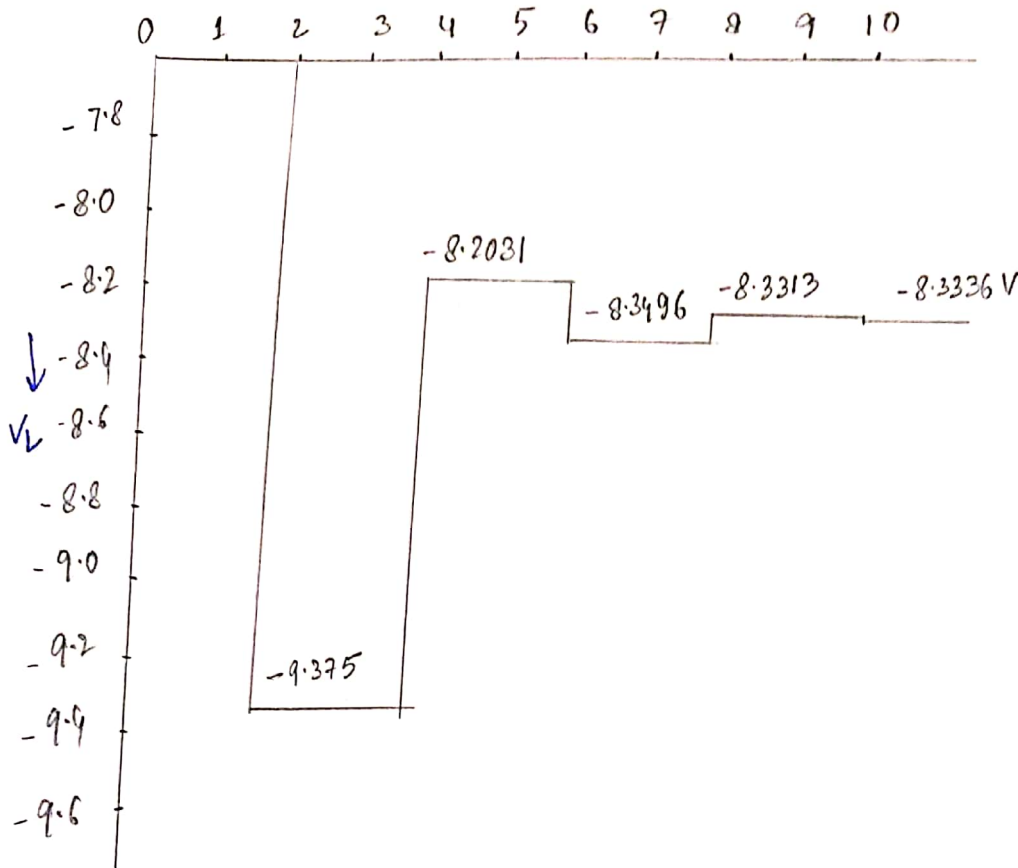
$$10T \leq t < 12T, V_L = -8.3313 - 0.0015 - 0.0008 = -8.3336 V.$$



3c)

$$T = 1 \mu s.$$

$$0 \leq t < T \Rightarrow V_L = 0.$$

$$T \leq t < 2T \Rightarrow V_L = 9.375 \text{ V}$$

$$2T \leq t < 3T \Rightarrow V_L = 0 \text{ V.}$$

$$3T \leq t < 4T \Rightarrow V_L = 8.2031 - 9.375 = -1.1719 \text{ V}$$

$$4T \leq t < 5T \Rightarrow V_L = 0 \text{ V.}$$

$$5T \leq t < 6T \Rightarrow V_L = 8.3496 - 8.2031 = 0.1465 \text{ V}$$

$$6T \leq t < 7T \Rightarrow V_L = 0 \text{ V}$$

$$7T \leq t < 8T \Rightarrow V_L = 8.3313 - 8.3496 = -0.0183 \text{ V}$$

$$8T \leq t < 9T \Rightarrow V_L = 0$$

$$9T \leq t < 10T; V_L = 8.3336 - 8.3313 = 0.0023 \text{ V}$$

$$10T \leq t < 12T, V_L = 0.$$

