

EE 931 - LECT. #11

FEB. 7, 2020

exam next friday.

from example #6 ( $Z_{in}$ )

$$Z_{in} = Z_0 \left[ \frac{Z_L + jZ_0 \tan(\beta x)}{Z_0 + jZ_L \tan(\beta x)} \right] [\Omega]$$

for short ckt load,  $Z_L = 0$ :

$$Z_{in}^{sc} = jZ_0 \tan(\beta x) [\Omega] \rightarrow \text{purely reactive}$$

$\uparrow$        $\uparrow$   
 real    react

for open ckt load,  $Z_L \rightarrow \infty$ 

$$Z_{in}^{oc} = -jZ_0 \cot(\beta x) [\Omega] \rightarrow \text{purely reactive}$$

2 useful things

1. C, L are reactive  $\rightarrow$  can use open-ckt'd or short-ckt'd line as inductor or capacitor!

2. cool trick

$$Z_{in}^{sc} \cdot Z_{in}^{oc} = (jZ_0 \tan(\beta x))(-jZ_0 \cot(\beta x)) = Z_0^2$$

$$\rightarrow Z_0 = \sqrt{Z_{in}^{oc} Z_{in}^{sc}} [\Omega]$$

$\lambda/4$  transformer {quarter-wave transformer}

consider  $l = \lambda/4$


$$\tan(\beta l) = \tan\left(\frac{2\pi}{\lambda} \cdot \frac{\lambda}{4}\right) = \tan\left(\frac{\pi}{2}\right) \rightarrow \infty$$

$$\begin{aligned} \rightarrow Z_{in} &= Z_0 \left\{ \frac{Z_L + jZ_0 \tan(\pi/2)}{Z_0 + jZ_L \tan(\pi/2)} \right\} = Z_0 \left\{ \frac{0 + jZ_0}{0 + jZ_L} \right\} \\ &= Z_0^2 / Z_L \end{aligned}$$

use  $\lambda/4$  trans to match real {resistive} load to  $\Gamma$ .



add  $\lambda/4$  trans w/  $Z_0'$

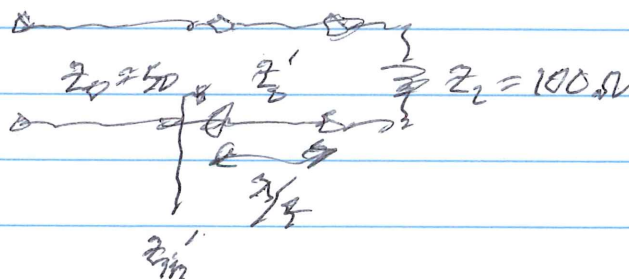

$$Z_{in}' = Z_0'^2 / Z_L \rightarrow 50 = \frac{Z_0'^2}{100}$$

$$\rightarrow Z_0' = \sqrt{(50)(100)} = 70.7 \Omega$$