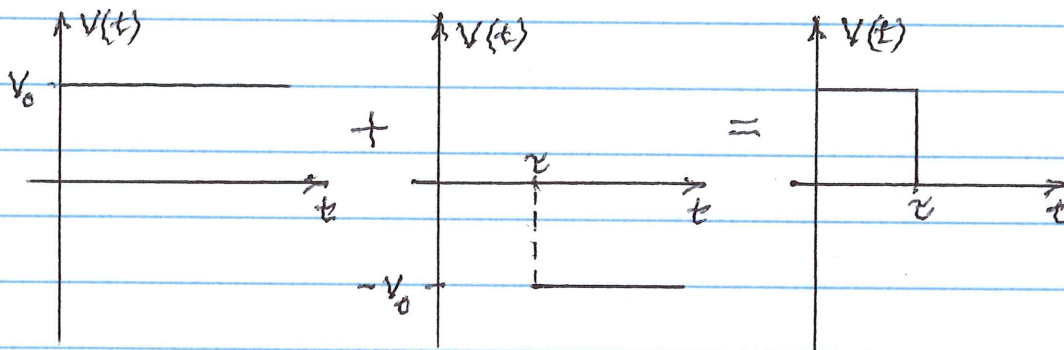


transients on a line


consider the sum of two step funcs:




these two step functions offset by time τ s.
result in a single pulse

can analyze what happens on a TL to a single
step func & combine results to get complete
behavior of pulse.

consider:

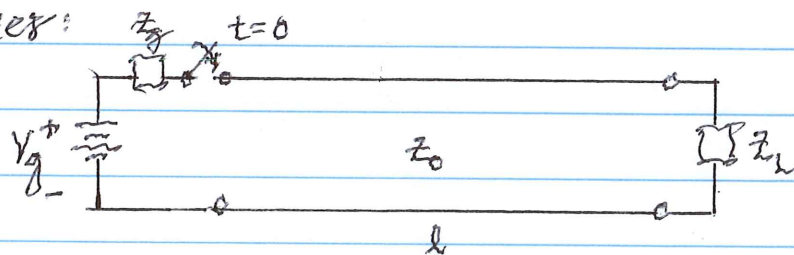

at $t = 0^+$

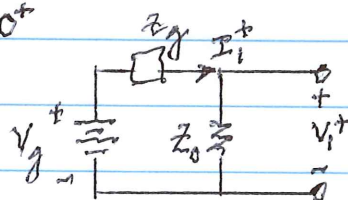

- Z_0 real for lossless line
- wave takes finite amt of time to travel to load

$$V_1^+ = \frac{z_0}{z_g + z_0} V_g \text{ [V]} \quad I_1^+ = \frac{V_g}{z_g + z_0} \text{ [A]}$$

wave travels down TL & reaches load at $t = T$.

$$T = l/u \text{ [s]}$$

at load, voltage (or curr) is sum of inc & refl voltage (or curr). thus,

$$@ t = T \quad V_L = V_1^+ + \Gamma_L V_1^+ = V_1^+ + V_1^- \quad \xrightarrow{T}$$

$\rightarrow \quad \leftarrow$

T seconds later refl voltage V_1^- hits generator.


voltage at gen is sum of initial voltages (i.e., we haven't turned off the generator), voltage reflected by load, and voltage reflected by mismatch of $z_g \neq z_0$ [Γ_g]. thus,

$$@ t = 2T \quad V_g = V_1^+ + V_1^- + \Gamma_g V_1^- = V_1^+ + \Gamma_L V_1^+ + \Gamma_g \Gamma_L V_1^+$$

$$= V_1^+ + V_1^- + V_2^+ \quad \xrightarrow{2T} \quad \xrightarrow{T}$$

$\rightarrow \quad \leftarrow \quad \rightarrow$
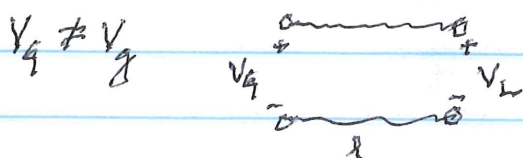
$$\Gamma_g = \frac{z_g - z_0}{z_g + z_0} \quad \Gamma_L = \frac{z_L - z_0}{z_L + z_0}$$



similarly,

$$@ t = 3T \quad V_L = V_1^+ + \Gamma_L V_1^+ + \Gamma_G \Gamma_L V_1^+ + \Gamma_L \Gamma_G \Gamma_L V_1^+$$

$$= V_1^+ + V_1^- + V_2^+ + V_2^- \quad \begin{array}{c} \xrightarrow{\quad} T \\ \xleftarrow{\quad} T \\ \xrightarrow{\quad} 3T \end{array}$$

$\frac{1}{2}$ so on. at steady state:


$$\begin{aligned} V_{\infty} &= V_1^+ + V_1^- + V_2^+ + V_2^- + V_3^+ + V_3^- + V_4^+ + \dots \\ &= V_1^+ (1 + \Gamma_L + \Gamma_G \Gamma_L + \Gamma_L \Gamma_G \Gamma_L + \Gamma_G \Gamma_L \Gamma_G \Gamma_L + \dots) \\ &= \text{geometric series} \end{aligned}$$

V_{∞} can be written as:

$$V_{\infty} = V_1^+ \left(\frac{1 + \Gamma_L}{1 - \Gamma_G \Gamma_L} \right)$$

use eqs for V_1^+ , Γ_L , $\frac{1}{2} \Gamma_G$ in V_{∞} , do algebra, $\frac{1}{2}$ end up with
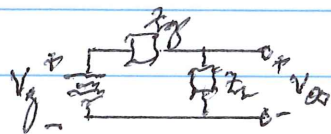
$$V_{\infty} = \frac{Z_L}{Z_g + Z_L} V_g, \quad I_{\infty} = \frac{V_g}{Z_g + Z_L}$$



at steady state get exactly what you'd get w/o a TL.

use bounce diagram to find behavior of transient before steady state is reached.