
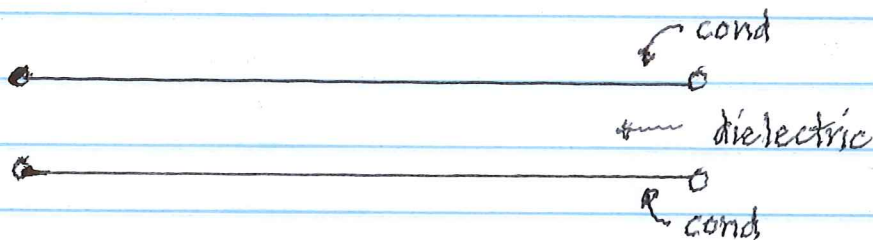


ch. 11 - transmission lines (TLs)

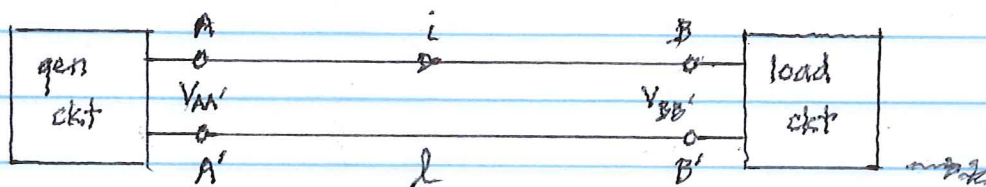we represent any two-conductor TL schematically by:



in ckt's, you considered the following set-up:



we connected a TL b/w gen ckt & load ckt &
then we ignored it. when can you ignore TL &
when can't you?

suppose:

$$V_{AA'} = V_0 \cos(\omega t)$$

what is $V_{BB'}$?

$$\begin{aligned} V_{BB'} &= V_0 \cos(\omega t - \beta l) & l &= \text{length of TL [m]} \\ &= V_0 \cos(\omega t - \beta l) & u &= \text{wave velocity [m/s]} \\ & & \beta &= \text{phase const [rad/m]} \end{aligned}$$

consider:

$$L = 2.5 \text{ cm } (\sim 1 \text{ in}) = \text{length of TL}$$

$$f = 2 \text{ kHz}$$

$$u = c = 3 \times 10^8 \text{ m/s}$$

$$\beta = \omega/u \text{ rad/m}$$

let $t = 0$, then

$$V_{AA'} = V_0$$

$$\begin{aligned} V_{BB'} &= V_0 \cos(2\pi f L / u) \\ &\approx 0.9999999999994517 V_0 \approx V_0 \end{aligned}$$

12 μs

seems okay to ignore TL.

consider:

$$L = 10 \text{ km} \approx 6.2 \text{ mi}$$

$$f = 2 \text{ kHz}$$

$$u = c = 3 \times 10^8 \text{ m/s}$$

find

$$\begin{aligned} V_{BB'} &\approx V_0 \cos(\beta L) \approx V_0 \cos(2\pi f L / u) \\ &\approx 0.9135 V_0 \end{aligned}$$

POTS (plain old telephone svc) $\sim 300 - 34 \text{ kHz}$

seems that we shouldn't ignore TL.

what's the difference? only λ , but relative to what? the wavelength.

in em, λ is an important concept. "define" problems by relative size of wavelength.

high freq problem: $\lambda \ll \text{object}$

low freq problem: $\lambda \gg \text{object}$

$$\lambda = 2\pi/\beta, \quad \beta = \omega/u = 2\pi f/u$$

$$\rightarrow \lambda = u/f \rightarrow f/\lambda = f/u$$

recall,

$$\beta l = 2\pi f l / u = 2\pi l / \lambda$$

$$\cos(\beta l) = \cos(2\pi l / \lambda)$$

rules of thumb:

$$l/\lambda \ll 1 \rightarrow \text{ignore TL}$$

$$l/\lambda \gtrsim 0.01 \rightarrow \text{may not be able to ignore TL.}$$