

in last lecture:

$$l/\lambda \ll 1 \rightarrow \text{ignore TL}$$

$$l/\lambda \gtrsim 0.01 \rightarrow \text{may not be able to ignore}$$

for $l = 2.5 \text{ cm}$, $f = 2 \text{ kHz}$:

$$l/\lambda \approx 1.7 \times 10^{-7} \ll 1$$

for $l = 10 \text{ km}$, $f = 2 \text{ kHz}$:


$$l/\lambda \approx 0.07 \gtrsim 0.01$$

power in U.S. $\rightarrow f = 60 \text{ Hz}$, for $u = c$ what is λ ?

$$\lambda = u/f = 5 \times 10^6 \text{ m} \approx 3107 \text{ mi}$$


lumped element model of TL

consider:

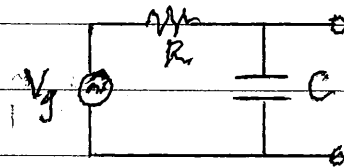


R, C , etc, are
lumped elements

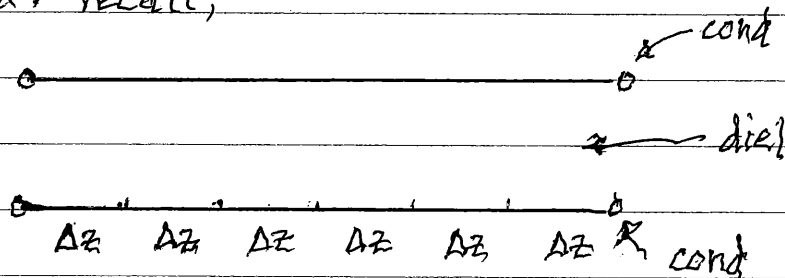TL's have R, C , etc, but distributed throughout TL,
not lumped. recall,



we break the line into tiny chunks Δz long.

consider one chunk:

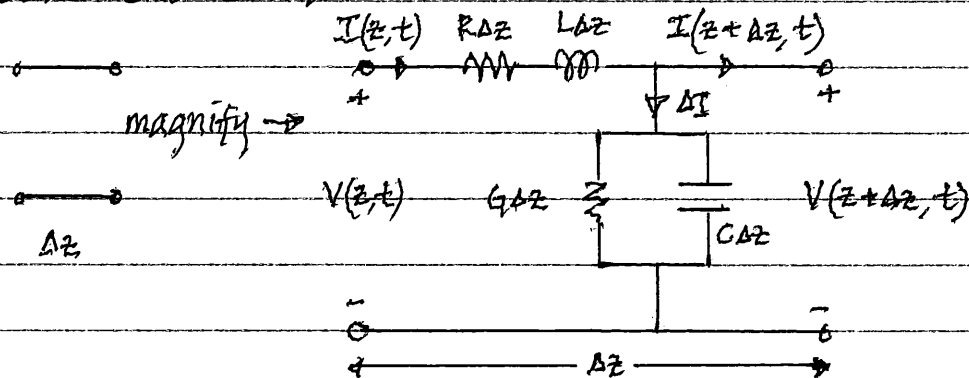

lumped element model

TL parameters

1. R, L, G, C

2. funcs only of physical properties of a TL,
i.e., the way they're made & for a fixed f
(table 11.1)

3. units in per meter

e.g., $R [\Omega/m]$ $R\Delta z = [\Omega/m][m] = [\Omega]$

A. 2 conductors $\rightarrow R, L$

- R = resistance (loss in conductors) $[\Omega/m]$

- L = inductance $[H/m]$

B. diel separating conductors $\rightarrow G$

- G = conductance (loss in dielectric) $[S/m]$

C. 2 conds + diel $\rightarrow C$

- C = capacitance $[F/m]$

derivation of TL eqs - want to find $V \& I$


$$\text{KVL: } V(z, t) \approx R \Delta z I(z, t) + L \Delta z \frac{\partial I(z, t)}{\partial t} + V(z + \Delta z, t)$$

rearrange & take limit as $\Delta z \rightarrow 0$

$$\lim_{\Delta z \rightarrow 0} \frac{V(z + \Delta z, t) - V(z, t)}{\Delta z} \approx R I(z, t) + L \frac{\partial I(z, t)}{\partial t}$$

$$\left\{ -\frac{\partial V(z, t)}{\partial z} = R I(z, t) + L \frac{\partial I(z, t)}{\partial t} \right\}$$

KCL:

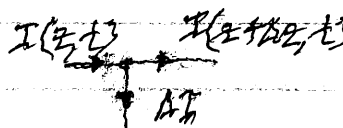

$$I(z, t) \approx \Delta I + I(z + \Delta z, t)$$

$$\begin{aligned} &= G \Delta z V(z + \Delta z, t) + C \Delta z \frac{\partial V(z + \Delta z, t)}{\partial t} \\ &\quad + I(z + \Delta z, t) \end{aligned}$$

rearrange & take limit:

$$\lim_{\Delta z \rightarrow 0} \frac{I(z + \Delta z, t) - I(z, t)}{\Delta z} \approx G V(z + \Delta z, t) + C \frac{\partial V(z + \Delta z, t)}{\partial t}$$

$$\left\{ -\frac{\partial I(z, t)}{\partial z} = G V(z, t) + C \frac{\partial V(z, t)}{\partial t} \right\}$$

these are the TL eqs . also called telegrapher's eqs

convert the TL eqs to phasor form.

$$V(z,t) = \operatorname{Re} \{ V_S(z) e^{j\omega t} \}$$

$$I(z,t) = \operatorname{Re} \{ I_S(z) e^{j\omega t} \}$$

$$\frac{\partial}{\partial t} \rightarrow j\omega$$

then,

$$-\frac{dV_S}{dz} = (R + j\omega L) I_S \quad (1)$$

$$-\frac{dI_S}{dz} = (G + j\omega C) V_S \quad (2)$$