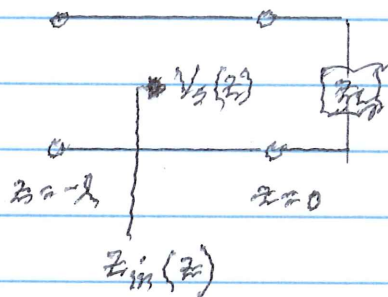


on Friday we found:

$$\begin{aligned} V_s(z) &= V_0^+ (e^{-\gamma z} + \Gamma_L e^{\gamma z}) \quad [V] \\ I_s(z) &= \frac{V_0^+}{Z_0} (e^{-\gamma z} - \Gamma_L e^{\gamma z}) \quad [A] \end{aligned} \quad \left\{ \begin{aligned} \Gamma_L &= |\Gamma_L| e^{j\theta_L} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \{-1\} \\ &= \text{voltage refl. coeff.} \end{aligned} \right.$$

now only 1 unknown - V_0^+

input impedance - differs from load



for now consider Z_{in} at $z = -l$.

$$V_s(-l) = V_0^+ (e^{\gamma l} + \Gamma_L e^{-\gamma l})$$

$$I_s(-l) = \frac{V_0^+}{Z_0} (e^{\gamma l} - \Gamma_L e^{-\gamma l})$$

$$Z_{in} = \frac{V_s(-l)}{I_s(-l)} = Z_0 \left(\frac{e^{\gamma l} + \Gamma_L e^{-\gamma l}}{e^{\gamma l} - \Gamma_L e^{-\gamma l}} \right)$$

recall,


$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$Z_{in} = Z_0 \left(\frac{e^{j\gamma l} + \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-j\gamma l}}{e^{j\gamma l} - \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-j\gamma l}} \right)$$

note that:

$$\frac{e^x + e^{-x}}{2} = \cosh x, \quad \frac{e^x - e^{-x}}{2} = \sinh x,$$

$$\tanh = \frac{\sinh x}{\cosh x}$$

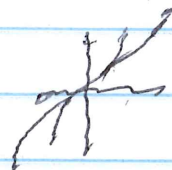


which (after a lot of algebra) =

$$Z_{in} = Z_0 \left(\frac{Z_L + Z_0 \tanh(j\gamma l)}{Z_0 + Z_L \tanh(j\gamma l)} \right) \quad [23]$$

= input impedance at start of TL

finding V_{in} - last unknown

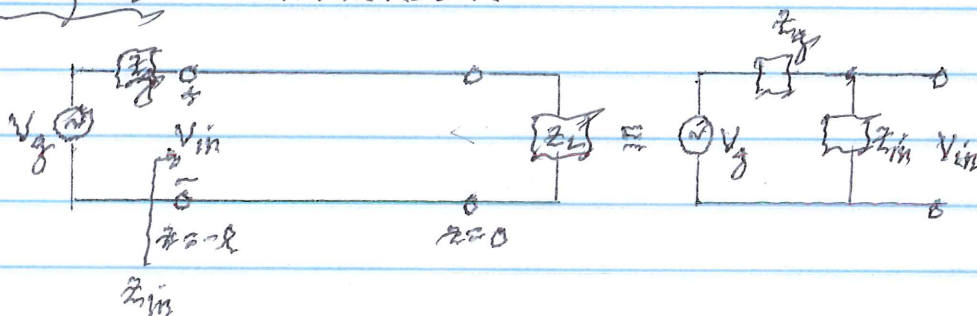

from ckt theory we can find V_{in} in terms of V_g using voltage divider:

$$V_{in} = \left(\frac{Z_{in}}{Z_{in} + Z_g} \right) V_g = V_g(-2)$$

$$\left(\frac{z_{in}}{z_{in} + z_g} \right) V_g = V_o^+ (e^{yL} + \Gamma_L e^{-yL})$$

solve for V_o^+ :

$$V_o^+ = \left(\frac{z_{in}}{z_{in} + z_g} \right) \frac{V_g}{(e^{yL} + \Gamma_L e^{-yL})} \quad \{V\} = \{V_o^+\} e^{j\omega t}$$

freq in ~~IDE~~